

Rudra Goel
Lab 03 Report
ECE 2031 L10
15 September 2024

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

-- Describes the device from the outside
entity RPS_VHDL is
-- Defines the signals coming into and out of the device
    port(
        R1, P1, S1  : in  std_logic;
        R2, P2, S2  : in  std_logic;
        W1, W2      : out std_logic;
        E1, E2      : out std_logic
    );
end RPS_VHDL;
-- Define the internal architecture of the device
architecture Internals of RPS_VHDL is
    -- Create a 6-bit vector -> gives us easy access to inputs
    signal all_inputs : std_logic_vector(5 downto 0);
begin
    -- "&" is CONCATENATION, not logical AND.
    all_inputs <= R1 & P1 & S1 & R2 & P2 & S2;
    -- Using a "selected signal assignment", aka "with/select"
    with all_inputs select W1 <=
        '1' when "100001",
        '1' when "010100",
        '1' when "001010",
        '0' when others;
    -- Using a "conditional signal assignment", aka "when/else"
    W2 <=
        '1' when all_inputs = "100010" else
        '1' when all_inputs = "001100" else
        '1' when all_inputs = "010001" else
        '0';
    -- Using when/else in a different way
    E1 <=
        '1' when (R1 = '1') and (S1 = '1') else
        '1' when (R1 = '1') and (P1 = '1') else
        '1' when (S1 = '1') and (P1 = '1') else
        '0';

    -- Using Boolean expression
    E2 <= (R2 and S2) or (R2 and P2) or (S2 and P2);
end Internals;

```

Figure 1. VHDL code to model a Rock-Paper-Scissor game between two players. “R1”, “S1”, “P1”, “R2”, “S2”, “P2” are inputs corresponding to rock, paper, and scissors for players one and two, respectively. Outputs “W1” & “W2” indicate which player wins. Outputs “E1” & “E2” indicate an invalid input combination for players one and two, respectively.

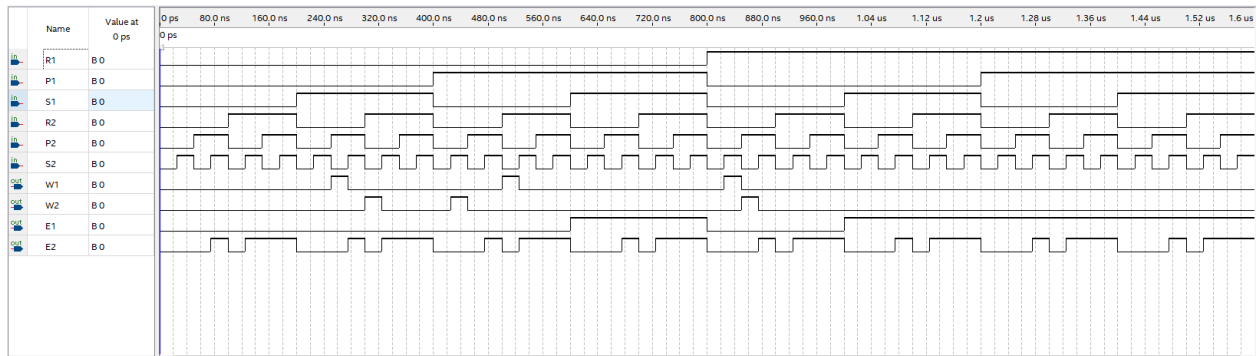


Figure 2. Waveform simulating all possible inputs for Rock-Paper-Scissor game between two players. “W1” goes high when player 1 wins & “W2” goes high when player 2 wins. “E1” and “E2” go high when players one or two put more than one of their dedicated inputs high.

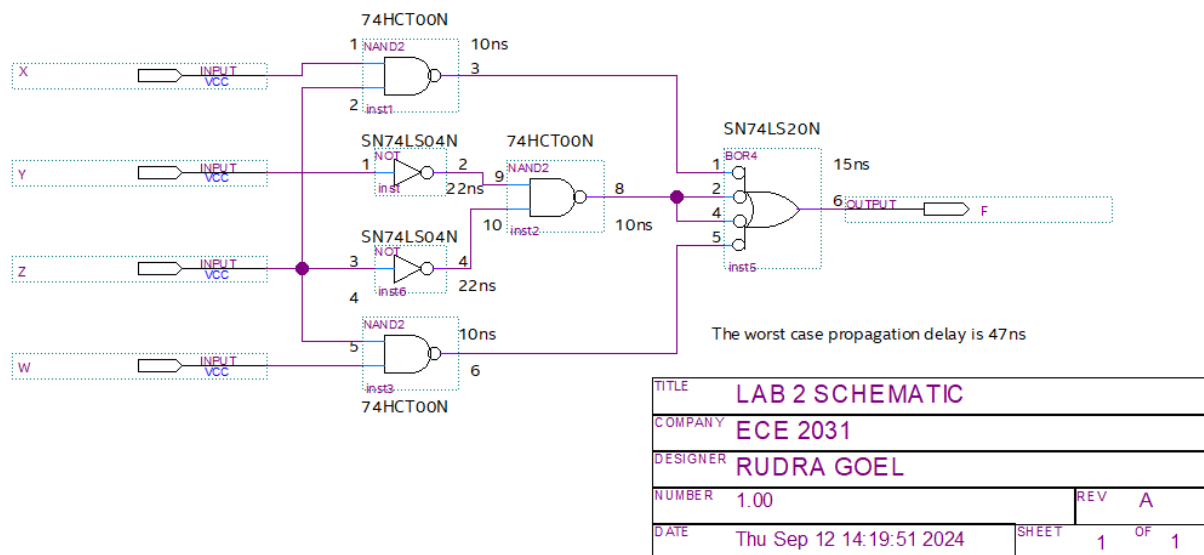


Figure 3. Schematic implementing $F = \overline{(\overline{Z} \cdot \overline{Y}) \cdot (\overline{X} \cdot \overline{Z}) \cdot (\overline{W} \cdot \overline{Z})}$ with propagation delays for each gate. The greatest propagation delay is 47ns from input “Y” to output “F”.

 


Figure 4. Square waveform of signal with period depending on equation: $\frac{\text{mod}(N,16) \cdot 4 + 455}{575 \div 53}$ where $N = 6$. Vertical cursors at each falling edge to measure period of $44.2\mu\text{s}$.

 


Figure 5. Oscilloscope capture of high time for square wave in Figure 2 meant to determine duty cycle. Vertical cursors measure high time to be $11.065\mu\text{s}$ thus indicating a 25% duty cycle.

 


Figure 6. Capture of falling edge of signal to determine fall time. Vertical cursors at intersections of 90% of high voltage and 10% high voltage to measure 3ns fall time.

 


Figure 7. High-to-Low propagation delay for input signal (brown) to output signal (green) for two in-series inverters. Vertical cursor at signal intersecting 1.3V measuring 13.9ns high-to-low delay.

 


Figure 8. Low-to-High propagation delay for input signal (brown) to output signal (green) for two in-series inverters. Vertical cursor at signal intersecting 1.3V measuring 14.4ns low-to-high delay.