
 


1. Demonstrate how a 4 bit ripple carry adder can be modified to a 4 bit subtractor with a single bit control (C), such that when $C = 0$, the circuit acts as an adder and when it is 1, the circuit acts as a subtractor.


Given a 4 Bit Ripple Carry adder

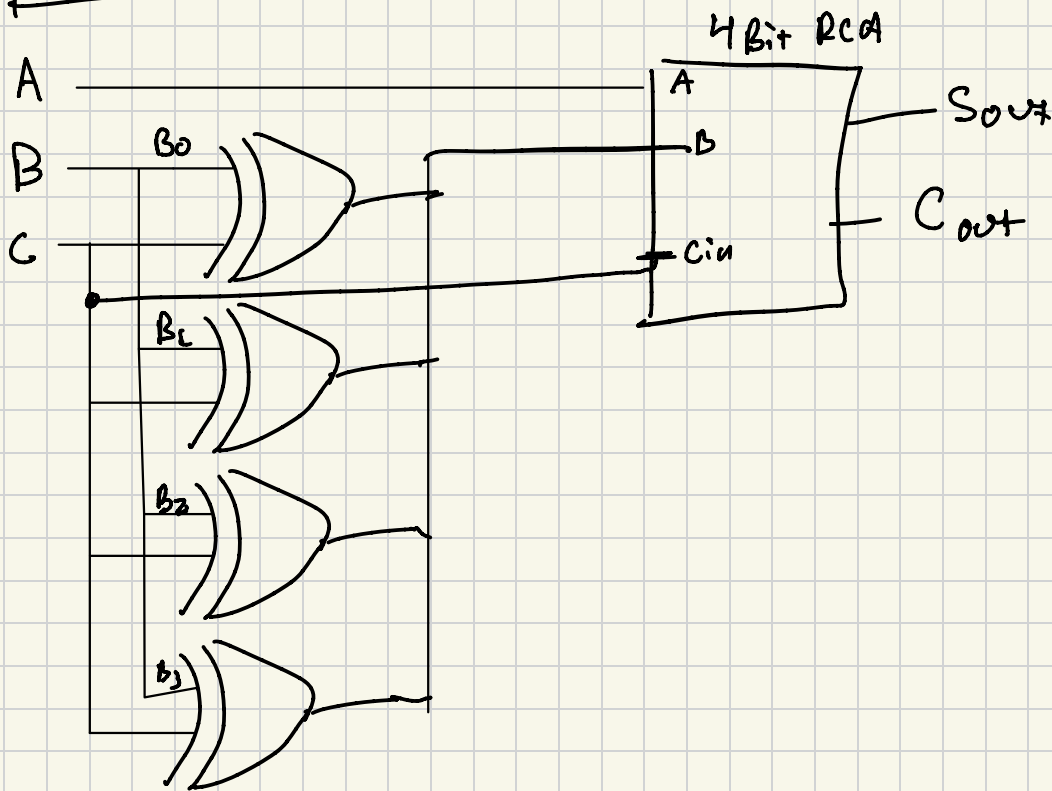

We can create a XOR Network on Input B



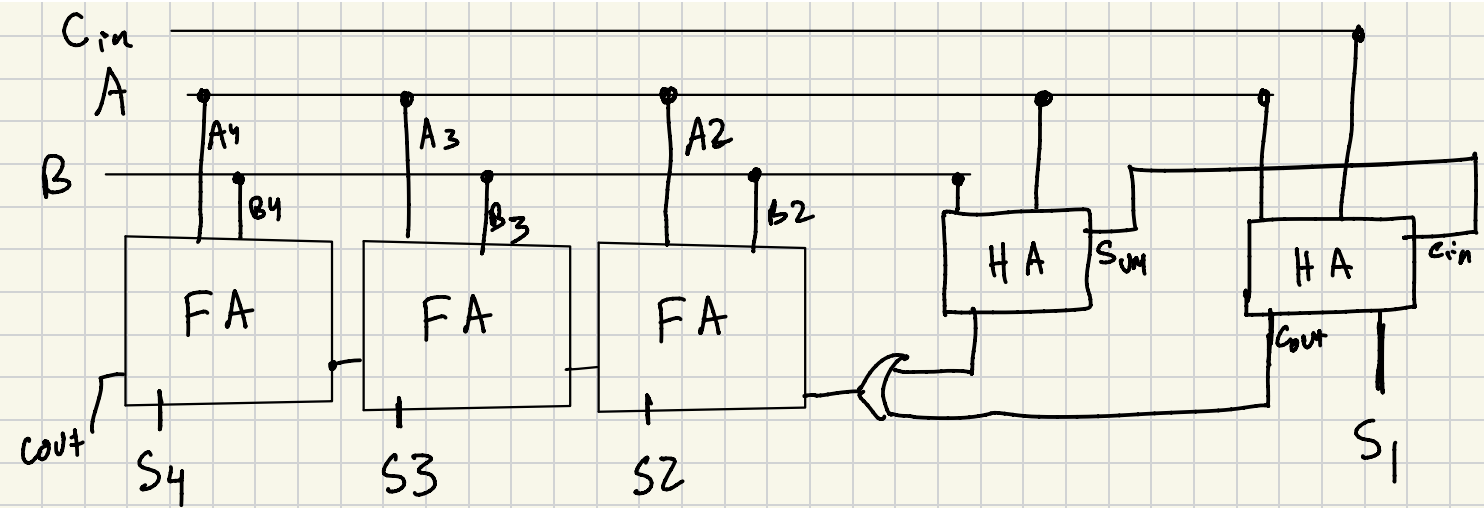2. Design a RippleCarry 4bit adder using 3 Full Adders, 2 Half Adders and an OR gate. You can draw full adders and half adders as blocks labeled with "FA" and "HA" respectively.



3. Calculate the worst-case delay of a 4-bit CLA where the delay of any gate can be approximated by $T = T_0 \cdot N^2$ where $T_0 = 1\text{ns}$ and N is the fan-in of the gate. Do not assume that the propagate and generate signals have already been generated.


The worst case delay of the 4 Bit CLA is generating the 4 Carryout C_4

Because $P + G$ is generated prior $\rightarrow C_4$ only is delayed (critical path of 5-input AND + 5-input OR)

$$1 \cdot 25 + 1 \cdot 25 = 50 \text{ ns}$$

$$P + G \text{ take } 1 \text{ ns each} \Rightarrow 50 + 1 = \boxed{51 \text{ ns}}$$

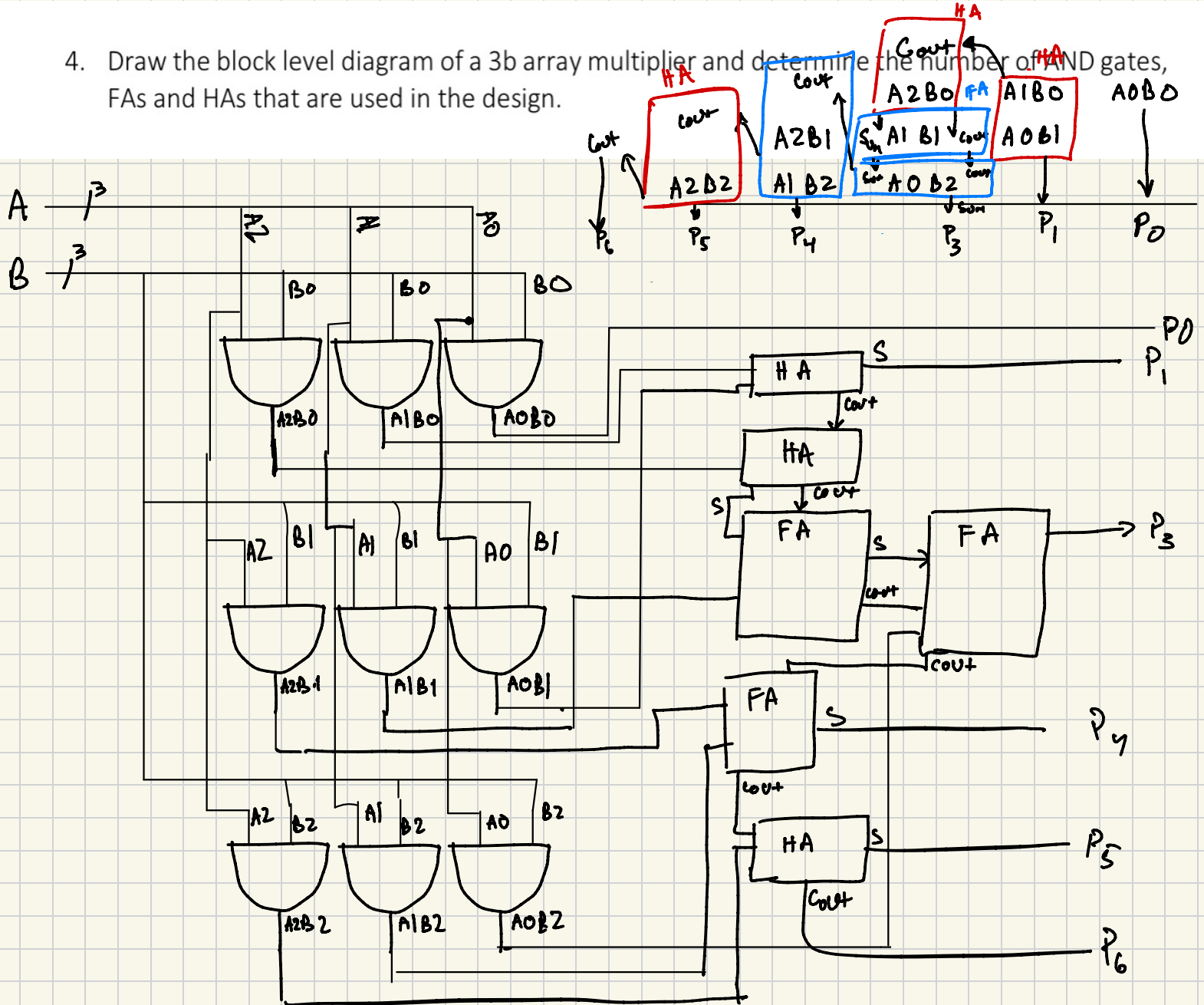4. Draw the block level diagram of a 3b array multiplier and determine the number of AND gates, FAs and HAs that are used in the design.



9 AND GATES
3 HALF ADDERS
3 FULL ADDERS

5. Perform 3×11 using the shift and add method in the 4 bit unsigned format. Fill up the following table.

$$(3)_{10} = (0011)_2$$

$$(11)_{10} = (1011)_2$$

Step (i)	Bi	A	Product Register State	Result

Step	Bi	A	Prod Reg	Res
0	1	1011	1011	1011
1	1	1011	10110	100001
2	0	1011	00000000	100001
3	0	1011	00000000	100001