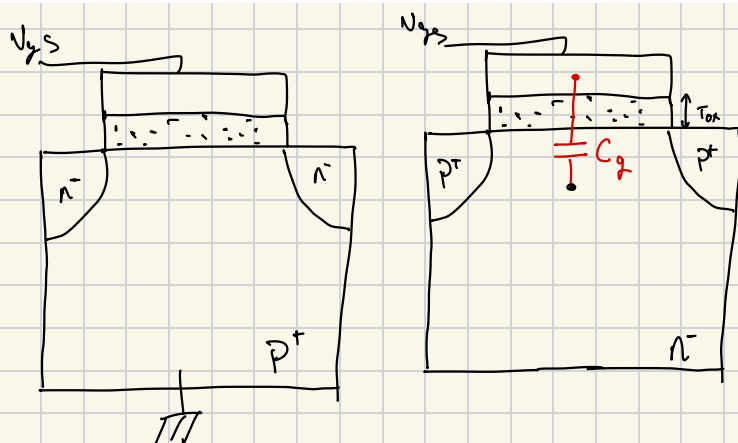


ECE 3150

Homework 2

- With the knowledge that $\mu_p = 0.4\mu_n$, what must be the relative width of the n-channel and p-channel MOS devices if they are to have equal drain currents when operated in the saturation mode with overdrive and drain-to-source voltages of the same magnitude. Also assume that the device lengths and oxide capacitances are equal.



The width of the n-channel MOSFET must be $\frac{4}{10}$ the width of the p-channel MOS device if they are to have same I_D @ saturation

When in saturation

$$I_{Dsat} = \frac{\beta V_{gt}^2}{2} \Rightarrow \beta = \frac{\epsilon_{ox} \mu}{t_{ox}} \left(\frac{W}{L} \right)$$
 for both in overdrive voltage

The oxide capacitances are equal


$$\Rightarrow \beta_{nmos} = \beta_{pmos} \Rightarrow \frac{\epsilon_{ox}}{t_{ox}} \mu_n (W_n) = \frac{\epsilon_{ox}}{t_{ox}} \mu_p (W_p)$$

$$\mu_n (W_n) = 0.4 \mu_n W_p$$

$$W_n = 0.4 W_p$$

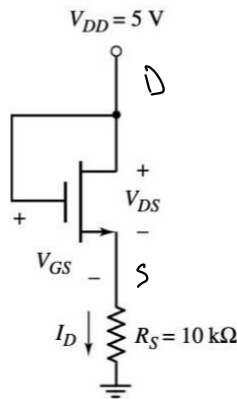2. Consider the MOS device shown in the picture below.

- Consider that $V_{GS} > V_T$ of the transistor. In which region of operation is the MOSFET operating?
- Given transistor parameters $V_T = 0.8V$ and $\beta = 0.1mA/V^2$, find out V_{GS} and I_D .



$$V_{GS} > V_T$$

$$V_{GS} - V_D$$

$$V_{DS} \quad V_{GS} - V_T$$

a) Since $V_{GS} = V_{DD}$ and $V_{DS} = V_{DD}$
 $\Rightarrow V_{DS} > V_{GS} - V_T$ Since $V_{GS} > V_T$
 $\Rightarrow V_{DS} \text{ is } > V_{GS} - V_T \Rightarrow \text{Device is}$
 in Saturation Region

$$b) I_D = \beta \frac{V_{GS}^2}{2} \Rightarrow \frac{V_S}{R_S} = I_D = \beta \frac{(V_G - V_S - V_T)^2}{2}$$

$$\frac{V_S}{10k} = \frac{0.1}{2} (4.2 - V_S)^2$$

$$= \frac{1}{10} V_S = 0.05 (4.2 - V_S)^2$$

$$V_S = 0.5 (4.2 - V_S)^2$$

$$V_{GS} = 2.866V$$

$$V_S = 2.134V \quad \checkmark$$


$$V_S = 8.266 \quad \times$$

$$\rightarrow V_G = 5$$

$$V_S = 2.134$$

$$I_D = \frac{V_S}{10k} \Rightarrow \frac{2.134}{10k} = 0.2134mA$$

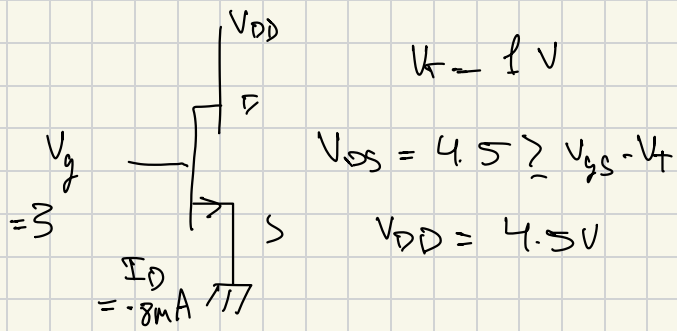3. An NMOS transistor with $V_T = 1V$ has a drain current of $0.8mA$ when $V_{GS} = 3V$ and $V_{DS} = 4.5V$. Calculate the drain current when (a) $V_{GS} = 2V$ and $V_{DS} = 4.5V$ and (b) $V_{GS} = 3V$ and $V_{DS} = 1V$.



$$I_D = \beta \frac{V_{gt}^2}{2} \Rightarrow$$

$$V_{gt} = 3 - 1 = 2$$

$$0.8 = \beta \frac{4}{2}$$

$$\boxed{1.4 = \beta}$$

a) $V_{GS} - V_T = 1 = V_{gt}$
 $V_{DS} > 2 - 1 \Rightarrow$

Saturation Region

$$I_{DS} = \beta \left(\frac{1^2}{2} \right) = \boxed{1.2mA}$$

b) $V_{GS} - V_T = 2$

$$V_{DS} < V_{GS} - V_T$$


$1 < 2 \Rightarrow$ Linear Region

$$I_D = \beta \left(V_{gt} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$= 1.4 \left(2 - \frac{1}{2} \right) (1) \Rightarrow 1.4 (1.5)$$

$$\boxed{I_D = 2.1mA}$$

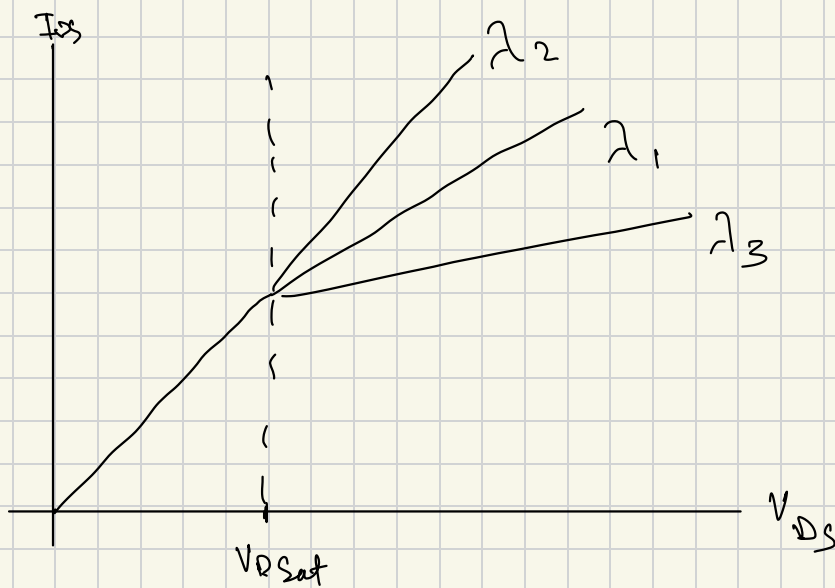4. If the saturation current of an NMOS device is given by: $I_{DS} = \frac{\beta}{2}(V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS})$. Draw the output characteristics of the device. What does λ signify? Assume $\lambda \ll 1/V_{DS}$.



$$I_{DS} = \frac{\beta}{2}(V_{GS} - V_T)^2 + \frac{\beta}{2}(V_{GS} - V_T)^2 \lambda V_{DS}$$

following the post reaching saturation stage ($V_{DS} > V_{GS} - V_T$) λ is the slope on I_{DS} for this region.

Given that V_{DS} in saturation is of second order, I_{DS} still rises linearly (λ)