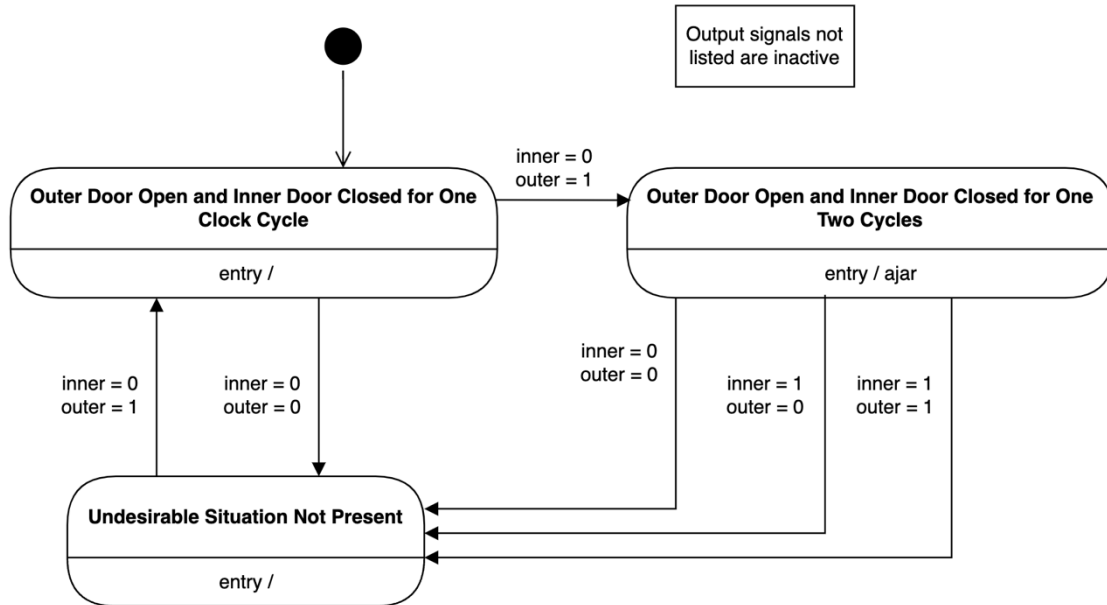



Rudra Goel  
Lab 04 Report  
ECE 2031 L10  
22 September 2024




**Figure 1.** A UML state diagram for a Moore state machine with two inputs (inner & outer) and one output (ajar) and two-bit state encodings. This machine alerts end-users via signal “ajar” when the outer door has been open (logic level 1), and the inner door has been closed (logic level 0) for two clock cycles.

Current State	Q1	Q0	inner	outer	Next State	Q1+	Q0+	ajar
Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0	0	Undesirable Situation Not Present	1	0	0
Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0	1	Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	0
Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	1	0	Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0
Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	1	1	Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0
Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	0	0	Undesirable Situation Not Present	1	0	1
Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	0	1	Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	1
Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	1	0	Undesirable Situation Not Present	1	0	1
Outer Door Open and Inner Door Closed for Two Clock Cycles	0	1	1	1	Undesirable Situation Not Present	1	0	1
Undesirable Situation Not Present	1	0	0	0	Undesirable Situation Not Present	1	0	0
Undesirable Situation Not Present	1	0	0	1	Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0
Undesirable Situation Not Present	1	0	1	0	Outer Door Open and Inner Door Closed for One Clock Cycle	0	0	0
Undesirable Situation Not Present	1	0	1	1	Undesirable Situation Not Present	1	0	0
unused	1	1	0	0	x	x	x	x
unused	1	1	0	1	x	x	x	x
unused	1	1	1	0	x	x	x	x
unused	1	1	1	1	x	x	x	x


**Figure 2.** State transition table for state machine defining behaviors of next state logic (Q1+ & Q0+) and output “ajar” for all possible input combinations for each state, both used and unused.

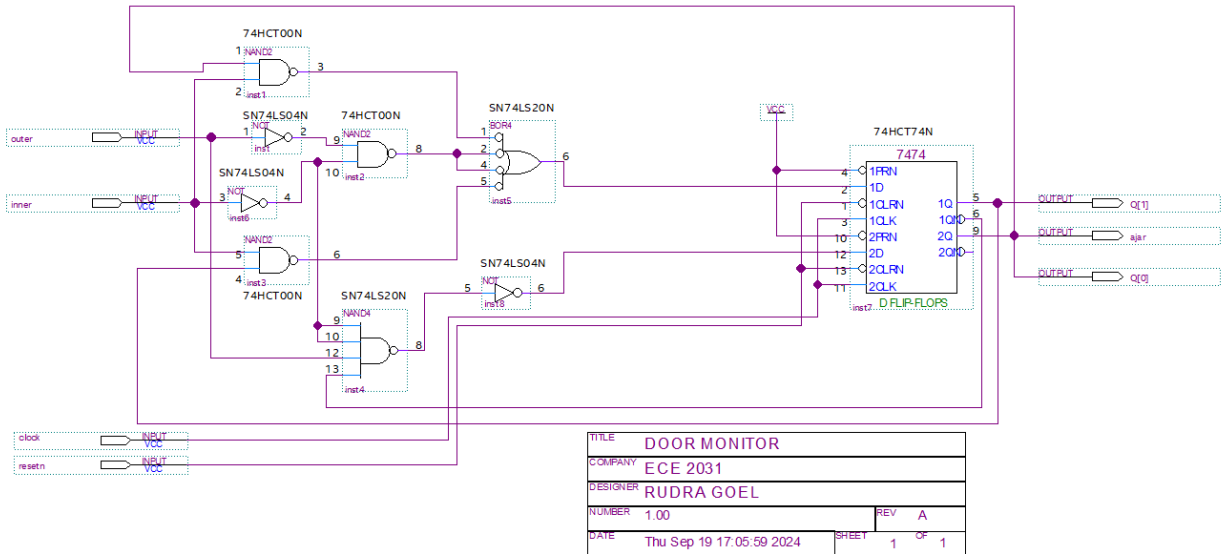


**Figure 3.** Schematic with pin assignments for the next state logic connected to dual flip flop IC to monitor current state. Inputs “inner”, “outer”, “clock” and “resetrn” (active low) and outputs “ajar”, “q1[1]” & “q0[0]” used as outputs to model a next state as a vectorized signal during waveform analysis.

 

**Figure 4.** Simulation of state machine illustrating functional schematic. Inputs “clock” oscillating at 50Hz. Output signal “ajar” only active after two rising-edge clock cycles of “outer” being logic high and “inner” being logic low. State machine resets to state “00” when input “resetrn” goes to logic low.

 

**Figure 5.** Completed breadboard circuit implementing state machine in actual hardware. Utilizing (left to right) SN74LS04N inverter, SN74HCT00N two-input NAND gate, SN74LS20N four-input NAND gate, and SN74HCT74N dual flip flop. LEDs used as active high to model “Q1” and “Q0” for current state.

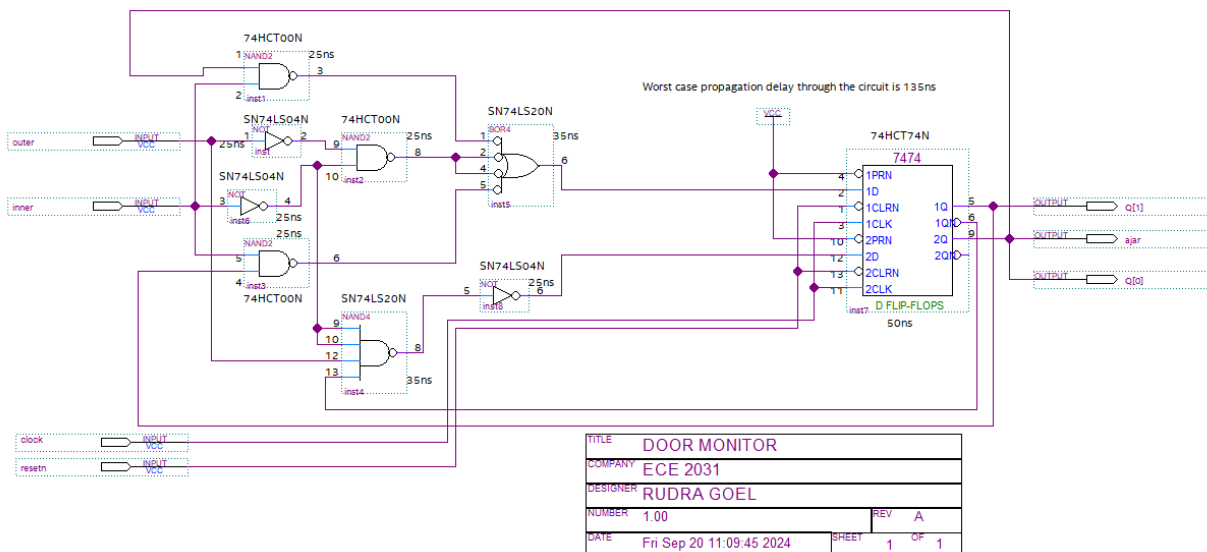

**Figure 6.** Schematic with propagation delays for each gate and clock-to-Q delay for flip flop. Worst case delay is 135ns from input “inner” to output “Q1.”