
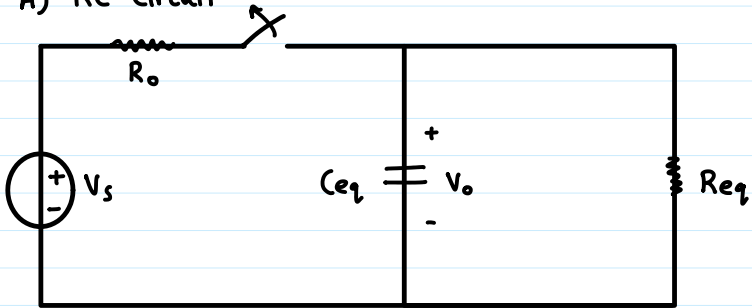



A) RC Circuit

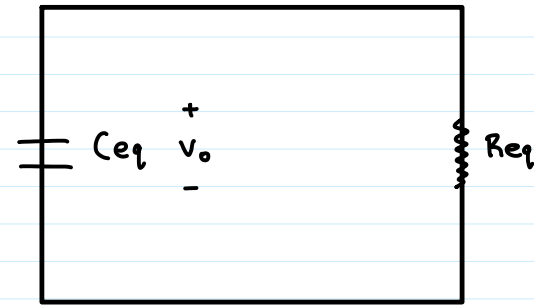


reduction

Prior to $t=0$, switch is closed.Prior to time $= 0$ ($t = 0^-$), switch is closed.Prior to time ≥ 0 ($t = 0^+$), switch is open.



B) RL Circuit

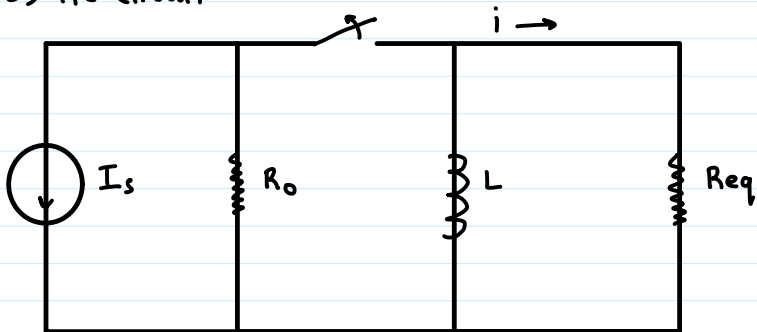

reduction

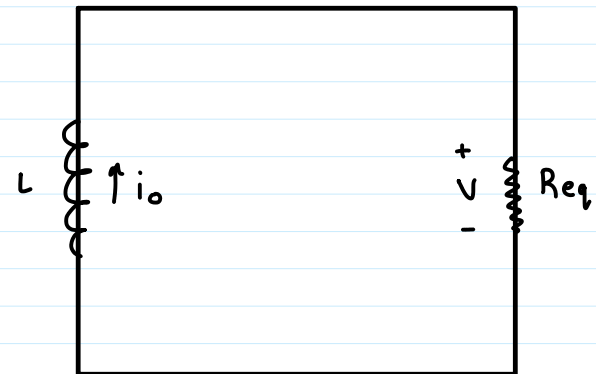

1)

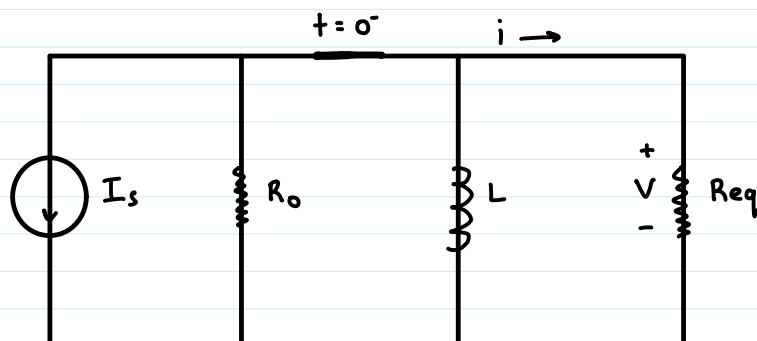
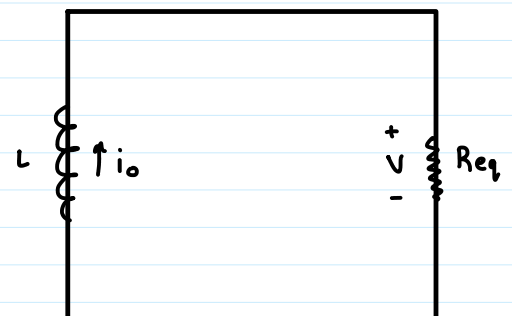
What is the natural response of circuit B at $t \geq 0$?circuit
reduction

$$V = L (di/dt)$$

$$V = 0$$

$t = 0^-$, current through \uparrow is I_s . ("Shunt") - small / little resistance

2)

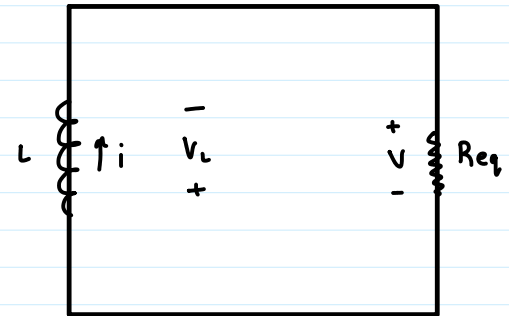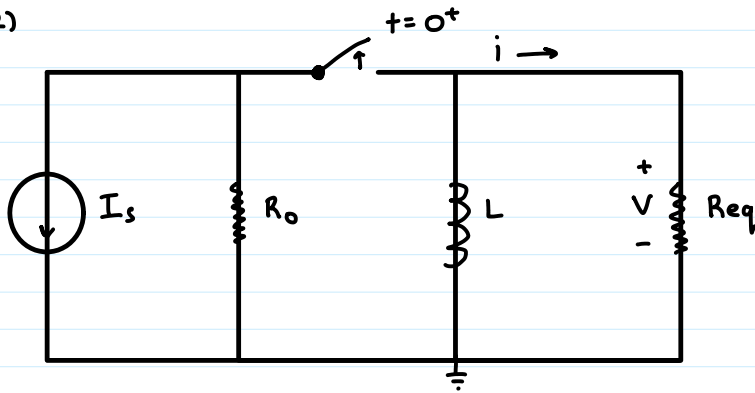

$$\text{KVL: } V_L + V = 0$$

$$L (di/dt) = V_L$$

$$\rightarrow L (di/dt) + Ri = 0 \quad (\text{differential equation}).$$

$$V = Ri$$

$$L (di/dt) + Ri = 0$$

$$\frac{di}{dt} = -\frac{Ri}{L}$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\int_{i(t=0)}^{i(t)} \frac{1}{x} dx = \int -\frac{R}{L} dt$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} t$$

$$e^{\ln(i(t)/i(0))} = e^{-\frac{R}{L} t}$$

$$i(t) = i(0) (e^{-\frac{R}{L} t})$$

$$i(0) = i(0^-) = i(0^+) = I_0$$

$$i(t) = I_0 e^{-\frac{R}{L} t}$$

$$\text{Ohm's Law: } V = IR$$

$$v(t) = I_0 R e^{-\frac{R}{L} t}$$

Ohm's Law: $V = IR$

$$V(t) = I_0 R e^{-\frac{R}{L}t}$$

$$V(0^-) = 0 \quad (\text{across inductor}).$$

$$V(0^+) = I_0 R.$$

*) Power dissipated in the resistor can be obtained from:

$$P = Vi = i^2 R = \frac{V^2}{R}$$

$$P = I_0 e^{-(R/L)t} I_0 e^{-(R/L)t} R$$

$$P = I_0^2 e^{-2(R/L)t}, \quad t \geq 0 \quad (t = 0^+)$$

Time constant (τ) (tau)


$$\tau = \frac{L}{R} \quad (\text{"tau"})$$

$$i(t) = I_0 e^{-t/\tau}$$

$$W(t) = \int_0^t P(x) dx = \int_0^t I_0^2 R e^{-2(R/L)x} dx$$

$$= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}), \quad t \geq 0, \quad t(0^+).$$

Example: RL Circuit


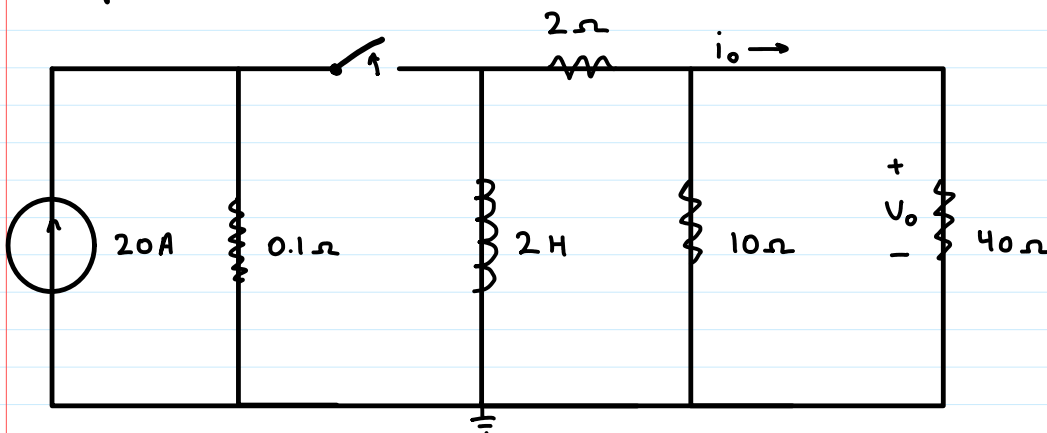


a) $i_L(t) = ?$ for $t \geq 0$.

$$i_L(t) = 20A$$

$$i_L(0^-) = i_L(0^+) = i_L(0)$$

b) $i_o(t) = ?$ for $t \geq 0^+$

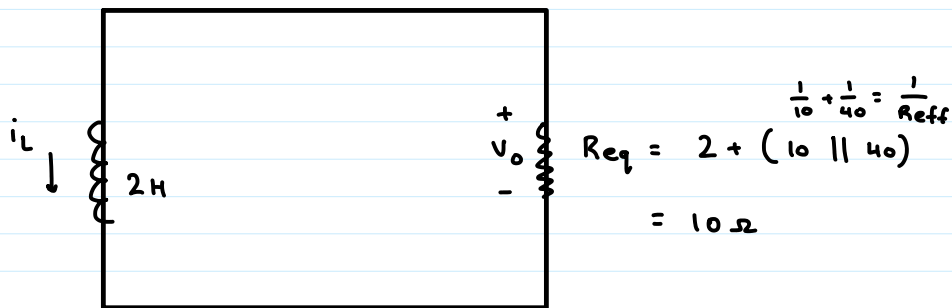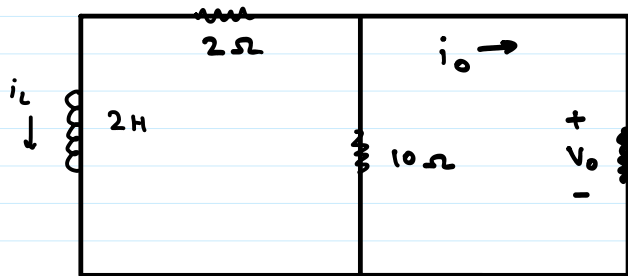

Time constant:

$$\tau = \frac{L}{R} = \frac{2}{10} = 0.2 \text{ seconds.}$$

Natural response:

$$i(t) = 20e^{-5t} \text{ A}, \quad t \geq 0^+$$

$$i_o = -i_L \left(\frac{10}{40 + 10} \right)$$

$$i_o(t) = -4e^{-5t} \text{ A}, \quad t \geq 0.$$

$$V_o(t) = 40(-4)e^{-5t} \text{ A}$$

$$V_o(t) = -160e^{-5t} \text{ A}$$

$$P_{10\Omega}(t) = \frac{V_o^2}{10}$$

$$= 2560 e^{-10t} \text{ W, } t \geq 0^+$$

$$\int_0^{\infty} P_{10\Omega}(t) dt = 256 \text{ J}$$

$$W_{\text{inductor}} = \frac{1}{2} L I^2(0) = 400 \text{ J}$$

$$i_0 = -i_L\left(\frac{1}{5}\right)$$

% energy dissipated by 10Ω $(256/400) \sim 64\%$.