

Midterm 2

Tuesday, November 19, 2024 12:47 PM



Midterm2_...

MID-TERM EXAM 2 Fall 2024

ECE 2040

NAME: Rudra Goel

MAJOR: *Computer Engineering*

INSTRUCTIONS

This is an open book exam. You are allowed to use your calculators and MATLAB.

This is a take-home exam (due date: November 23, 2024, by 11:59 PM).

Upload a copy of your completed exam to canvas.

LATE SUBMISSIONS ARE NOT ALLOWED.

Please note that solutions similar to those of other students in the class will NOT be graded.

2

Problem 1 (20 points). Assume that the numerical values for the signal voltage in Fig. 1 are $V_m = 50$ mV and $t_1 = 1$ s. This signal voltage is applied to the integrating-amplifier circuit shown in Fig. 2. The circuit parameters of the amplifier are $R_s = 100K\Omega$, $C_f = 0.1\mu\text{F}$, and $V_{ec} = 6$ V. The initial voltage on the capacitor is zero.

- (a) Calculate $V_o(t)$.
(b) Plot $V_o(t)$ versus t .

$$V_s(t) = \begin{cases} 50 \text{ mV} & 0 \leq t \leq 1 \\ -50 \text{ mV} & 1 \leq t \leq 2 \end{cases}$$

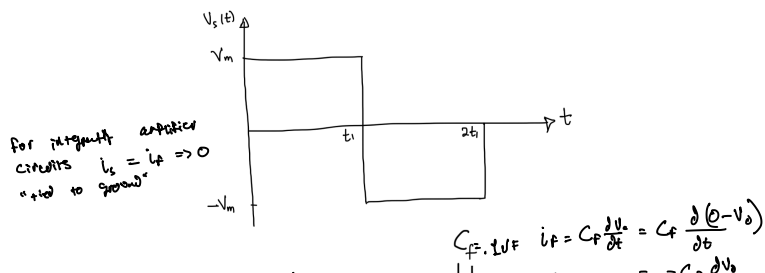


Fig. 1.

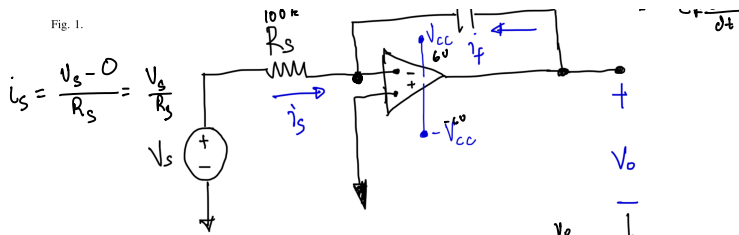


Fig. 2.

$$i_s = i_f$$

$$\Rightarrow \frac{V_s}{R_s} = -C_f \frac{dV_o}{dt}$$

$$\int_0^t \frac{1}{R_s} dt = -\int_0^t C_f \frac{dV_o}{dt} dt$$

$$\Rightarrow -\frac{1}{C_f R_s} \int_0^t V_s dt = \int_0^t \frac{dV_o}{dt} dt$$

$$a) V_o(t) = -\frac{1}{C_f R_s} \int_0^t V_s dt \Rightarrow \begin{cases} -\frac{1}{C_f R_s} (50e-3) t & 0 \leq t \leq 1 \\ -\frac{1}{C_f R_s} (50e-3) + 1 & 1 \leq t \leq 2 \end{cases}$$

$$\frac{1}{C_f R_s} = 100$$

$$V_o(t) = \begin{cases} -5t & 0 \leq t \leq t_1 \\ 5t - 10 & t_1 \leq t \leq t_2 \end{cases}$$

Problem 2 (20 points). At the instant the switch makes contact with the terminal **a** in Fig. 3, the voltage on the 0.1 μF capacitor is 5 V. The switch remains at terminals **a** for 9 ms and then moves instantaneously to terminal **b**. How many milliseconds after making contact with the terminal **a** does the operational amplifier saturate?

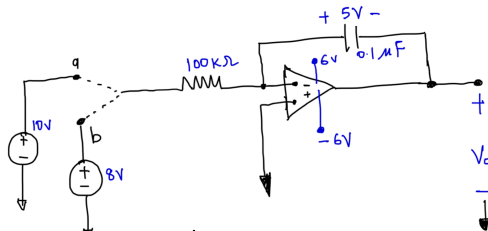


Fig. 3.

$$V_o(t) = -\frac{1}{C_f R_s} \int_0^t V_{in} dt \Rightarrow -\frac{1}{C_f R_s} \int_0^t 10 dt$$

$$V_o(9) = -1000(1.009) + 5 = -4 \text{ volts}$$

$$\textcircled{1} \frac{-10}{.01} (t) + C$$

Initial voltage on capacitor

$$V_o(t) = -1000t + 5 = -6$$

$$-1000t = -11$$

$$t = \frac{11}{1000} = .011$$

$$t = 11 \text{ ms}$$

Does not saturate @ 9 ms
→ saturates @ 11 ms

When switch to B

$$\textcircled{2} V_o(t) = -\frac{1}{C_f R_s} \int_0^t 8 dt$$

$$V_o = -\frac{8}{.01} t - 4$$

$$-6 + 4 = -800t \Rightarrow t = 25 \text{ ms} + 9 \text{ ms} = 34 \text{ ms}$$

11.5 ms till saturation

Problem 3 (20 points). A sequential switching circuit is shown in Fig. 4. The two switches shown in the circuit have been closed for a long time. At $t = 0$, switch 1 is opened. Then 35 ms later, switch 2 is opened. Assume that $i_a = i_b$, $R_1 = 10 \Omega$, $R_2 = 10 \Omega$, $R = 10 \Omega$, $V_{cc} = 15 \text{ V}$, $R_{load} = 40 \Omega$. Note that Q_1 is an npn bipolar junction transistor.

- (a) Find $i_L(t)$ for $0 \leq t \leq 35 \text{ ms}$.
 (b) Find $i_L(t)$ for $t \geq 35 \text{ ms}$.
 (c) What percentage of the initial energy stored in the 150 mH inductor is dissipated in the 18 Ω resistor?

$$\textcircled{1} i_a = i_o, i_b = \frac{V_{cc} - V_a}{R}$$


$$i_o = \frac{V_a}{R_{load}} = i_a$$

$$\frac{V_{cc} - V_a}{R} = \frac{V_a}{R_{load}}$$

$$\Rightarrow \frac{V_a R}{R_{load}} + V_{cc} = V_a$$

$$\Rightarrow \text{Since } V_a = V_b$$
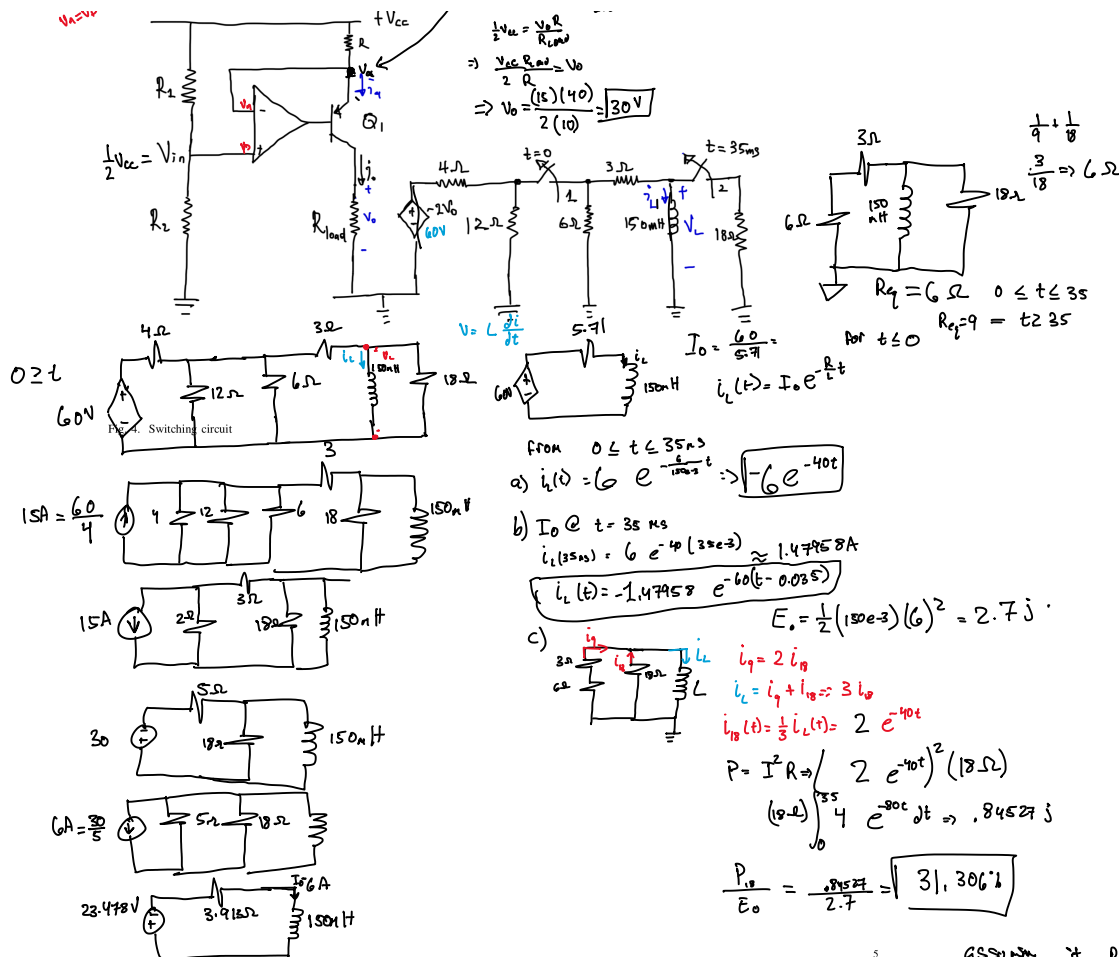
$$V_b = \frac{1}{2} V_{cc} = \frac{V_{cc} - V_b R}{R_{load}}$$



Problem 4 (20 points). The circuit shown in Fig. 5 stems from the concatenation of a realistic (non-ideal) non-inverting operational amplifier model and an RC circuit. The switch in the circuit has remained in position 1 for a long time. At $t = 0$, the switch moves to the position 2. If $R_s = 1000\Omega$, $R_f = 3000\Omega$, $R_g = 1000\Omega$, $R_i = 75\text{M}\Omega$, $R_o = 50\Omega$, $A = 10^5$ and $V_g = 10V$, find the following:

- (a) $V_o(t)$ for $t \geq 0$
 (b) $i_o(t)$ for $t \geq 0^+$

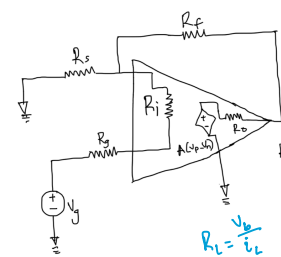


Fig. 5.

a) $\sum V = 0 \Rightarrow V_o - 40k \left((1.25e-6) \frac{dV}{dt} \right) + 60 = 0$

$V_o + 60 - 0.01 \frac{dV}{dt} = 0$

$\frac{dV}{dt} - 100V_o = 6000$

Integrating: $e^{\int -100 dt} \Rightarrow e^{-100t}$

$\int e^{-100t} \frac{dV}{dt} - 100 e^{-100t} V_o = \int 6000 e^{-100t} dt$

$\Rightarrow e^{-100t} V_o = (6000) \left(\frac{-1}{100} \right) \int e^{-100t} dt$

$e^{-100t} V_o = -60 e^{-100t} + C$

$V_o = -60 + C e^{100t}$

$30 = -60 + C e^0 \Rightarrow C = 90$

$V_o = 90 e^{-100t} - 60$


b) $i_o(t) = \frac{V_o(t)}{R_o} = \frac{90 e^{-100t} - 60}{40k}$

5

Assuming it behaves like an ideal op.

$V_o = \left(1 + \frac{R_f}{R_i} \right) V_g$

$= 4 V_g = 40V$

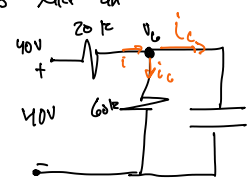

$\left(\frac{20k}{20k + 60k} \right) 40 = \frac{1}{4} (40) = 30V @ V_o$

$V_o = \left(\frac{20k}{20k + 60k} \right) V_b$

$V_o = \frac{V_b}{4}$

$R_{eq} = \left(\frac{R_o}{1 + \frac{R_o}{R_i}} \right)^{-1}$

$\left(\frac{80 + R_i}{80 R_L} \right)^{-1}$

$R_{eq} = \frac{80 R_L}{80 + R_i}$

$V_o = V_{oc} - (V_{oc} - V_o) e^{-t/\tau}$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

$V_o = 30V$

6

Problem 5 (20 points). A custom circuit for strain measurement in solids can be found in Fig. 6. For this circuit, do the following:

(a) (15 points) Prove that the relationship between the input and output voltages can be expressed as:

$$V_o = \frac{R_f (2\Delta R)}{R^2 - (2\Delta R)^2} V_{ref} \quad (1)$$

(b) (5 points) If $R = 120 \Omega$ with $\delta = \frac{\Delta R}{R} = 0.01$, and the power supplies to the op-amp are $\pm 15 \text{ V}$ with the reference voltage V_{ref} taken from the positive power supply. Calculate the value of R_f if the output voltage is 5 V.

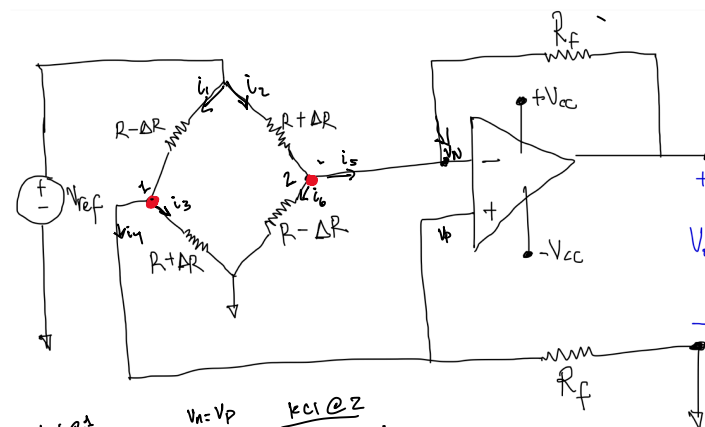


Fig. 6.

$$\begin{aligned} \text{KCL @ 1: } -i_1 + i_3 + i_4 &= 0 & V_N &= V_P & \text{KCL @ 2: } -i_2 + i_5 + i_6 &= 0 \\ \frac{-(V_{ref} - V_P)}{R - \Delta R} + \frac{V_P}{R + \Delta R} + \frac{V_P}{R_f} & & \frac{-(V_{ref} - V_N)}{R + \Delta R} + \frac{-(V_o - V_N)}{R_f} + \frac{V_N}{R - \Delta R} &= 0 \end{aligned}$$

$$\frac{V_P - V_{ref}}{R - \Delta R} + \frac{V_P}{R + \Delta R} + \frac{V_P}{R_f} = 0$$

$$\frac{(V_P - V_{ref})(R + \Delta R)R_f + V_P(R - \Delta R)(R_f) + V_P(R + \Delta R)(R - \Delta R)}{(R - \Delta R)(R + \Delta R)R_f}$$

$$\frac{V_p (R + \Delta R)(R_f) - V_{ref} (R + \Delta R)(R_f) + V_p (R - \Delta R)(R_f) + V_p (R + \Delta R)(R - \Delta R)}{(R - \Delta R)(R + \Delta R)R_f}$$

$$V_p \left[(R + \Delta R)(R_f) + (R - \Delta R)(R_f) + (R + \Delta R)(R - \Delta R) \right] - V_{ref} (R + \Delta R)(R_f) = 0$$

$$(1) \quad V_p = \frac{V_{ref} (R + \Delta R)(R_f)}{(R + \Delta R)(R_f) + (R - \Delta R)(R_f) + (R + \Delta R)(R - \Delta R)}$$

$$\frac{V_n (R + \Delta R)}{R - \Delta R} + \frac{V_n - V_{ref}}{R + \Delta R} + \frac{V_n - V_o}{R_f} = 0$$

$$V_n (R + \Delta R)R_f + (V_n - V_{ref})(R - \Delta R)R_f + (V_n - V_o)(R + \Delta R)(R - \Delta R) = 0$$

$$V_n (R + \Delta R)R_f + V_n (R - \Delta R)R_f - V_{ref} (R - \Delta R)R_f + V_n (R + \Delta R)(R - \Delta R) - V_o (R + \Delta R)(R - \Delta R) = 0$$

$$V_n \left[(R + \Delta R)R_f + (R - \Delta R)R_f + (R + \Delta R)(R - \Delta R) \right] - V_{ref} (R - \Delta R)R_f + V_o (R + \Delta R)(R - \Delta R) = 0$$

$$(2) \quad V_n = \frac{V_{ref} (R - \Delta R)R_f + V_o (R + \Delta R)(R - \Delta R)}{(R + \Delta R)R_f + (R - \Delta R)R_f + (R + \Delta R)(R - \Delta R)} \quad V_p = V_n$$

$$\frac{V_{ref} (R + \Delta R)(R_f)}{(R + \Delta R)(R_f) + (R - \Delta R)(R_f) + (R + \Delta R)(R - \Delta R)} = \frac{V_{ref} (R - \Delta R)R_f + V_o (R + \Delta R)(R - \Delta R)}{(R + \Delta R)R_f + (R - \Delta R)R_f + (R + \Delta R)(R - \Delta R)}$$

$$\frac{(V_{ref})(R + \Delta R)(R_f) \left[\cancel{(R + \Delta R)R_f} + \cancel{(R - \Delta R)R_f} + \cancel{(R + \Delta R)(R - \Delta R)} \right]}{\cancel{(R + \Delta R)R_f} + \cancel{(R - \Delta R)R_f} + \cancel{(R + \Delta R)(R - \Delta R)}} - V_{ref} (R - \Delta R)R_f = V_o (R + \Delta R)(R - \Delta R)$$

$$\frac{V_{ref} (R + \Delta R)(R_f) - V_{ref} (R - \Delta R)R_f}{(R + \Delta R)(R - \Delta R)} = V_o$$

$$V_o = \frac{V_{ref} R_f \left[(R + \Delta R) - (R - \Delta R) \right]}{R^2 - \Delta R^2} \Rightarrow \frac{V_{ref} R_f (2 \Delta R)}{R^2 - \Delta R^2}$$

$$b) \quad V_o = 5 \quad \frac{\Delta R}{R} = .01 \quad \begin{matrix} R = 120 \\ \Delta R = 1.2 \end{matrix}$$

$$\frac{(V_o)(R^2 - \Delta R^2)}{V_{ref} (2 \Delta R)} = R_f$$

$$\frac{(5)(120^2 - 1.2^2)}{15(2.4)} = R_f = 1,999.8 \Omega$$

