

AUDRA GORE

Maj: Computer engineering

Date: 12/9/2024

GTID: 903 897740

ECE 2040 Final exam  
Submission



**Problem 1.** Mark the following statements as either **True** or **False**

- (a) **True or False:** An LC circuit (with a DC source) is an oscillatory circuit.

(b) **True or False:** A circuit response may grow, rather than decay exponentially with time.

(c) **True or False:** The time constant of an RC circuit is  $\tau = \frac{1}{RC}$  while the time constant of an RL circuit is  $\tau = \frac{L}{R}$ .  

$$\tau = RC \Rightarrow \tau = \frac{L}{R}$$

(d) **True or False:** Kirchhoff's current and voltage laws hold in a frequency domain representation of an RLC circuit with a DC source.  

$$V = I \cdot Z_{\text{RLC}} \quad Z_R, Z_C, Z_L$$

(e) **True or False:** The decay constant  $\alpha$  in an **overdamped** system can also be referred to as a **damping factor** or a **damping coefficient**.

(f) **True or False:** The overall gain of two contiguous connected or concatenated summing amplifiers is equal to product of gain of each amplifier.  
**ACM SIM**

(g) **True or False:** A noninverting amplifier is an op amp circuit producing an output voltage that is a negative, scaled replica of the input voltage.

(h) **True or False:** Impedances in parallel share a common voltage.

(i) **True or False:** An attenuator is a passive device that affect its input power such that the output power is less than the input power. If the aforementioned fact is true, then this type of passive device can be fabricated from a network of resistors.

(j) **True or False:** Two voltage sources/supplies have +5 V, and -5 V terminals only. If these devices are connected such that the -5 V terminal from device 1 is connected to the +5 V terminal from device 2 then the device combination can be considered as a three terminal device with the common ground being the joint terminals.

(k) **True or False:** The capacitor does not allow sudden changes in voltage.

(l) **True or False:** The voltage applied to a 212 mH inductor in a circuit can be denoted as  $V(t) = 15e^{-5t}$  V. The current in the circuit is  $11.27e^{-10t}$  A.  

$$V = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int V dt \Rightarrow I = \frac{1}{L} \int 15e^{-5t} dt$$

(m) **True or False:** An inductor works as an open circuit if the circuit is powered by a DC source.

(n) **True or False:** A capacitor can be used in place of a resistor in a circuit with a high frequency input AC source.  

$$Z_L \neq Z_C \Rightarrow R \neq \frac{-j}{\omega C}$$

(o) **True or False:** The insulating medium between the two plates of capacitor is known as a capacitive medium.  
**"Dielectric"**

$$\tau = RC \quad \Rightarrow \quad t/v$$

$$V = I \cdot Z_{\text{eq}} \quad Z_R, Z_C, Z_L$$



A diagram of a capacitor consisting of two parallel plates. The top plate is labeled with a positive sign (+) and the bottom plate with a negative sign (-). A horizontal line extends from the top plate to the right, ending in a small circle containing the letter 'Q'. Another horizontal line extends from the bottom plate downwards.

$$\begin{aligned} v &= -5^t \\ dv &= -5^t \ln 5 \end{aligned}$$

(p) When the input voltage difference is small in magnitude, the operational amplifier behaves as linear

- (i) Non-linear device
- (ii) Complex device
- (iii) Linear device
- (iv) Bipolar device

(q) The condition for a Non-inverting amplifying circuit to function in linear region operation is  $\left(\frac{R_s + R_f}{R_s}\right) V_g < |V_{cc}/V_g|$


- (i)  $(R_s + R_f)/R_s < |V_{cc}/V_g|$
- (ii)  $(R_s + R_f)/R_s \neq |V_{cc}/V_g|$
- (iii)  $(R_s + R_f)/R_s > |V_{cc}/V_g|$
- (iv)  $(R_s + R_f)/R_s = |V_{cc}/V_g|$

$$\left(\frac{R_s + R_f}{R_s}\right) V_g < |V_{cc}/V_g|$$

output voltage

(r) All the rules and laws of D.C. circuit also apply to A.C. circuit containing

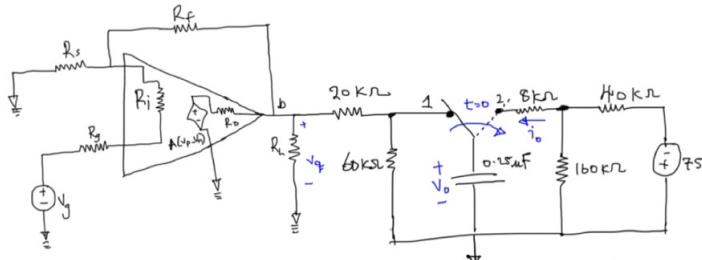- (i) Capacitance only
- (ii) Inductance only
- (iii) Resistance only
- (iv) all the above



$$i = C \frac{dV}{dt}$$

$$\int v = \int i dt$$

Fig. 1.  $v = \frac{1}{C} \int i dt$

(s) The circuit shown in Fig. 1 stems from the concatenation of a realistic (non-ideal) non-inverting operational amplifier model and an RC circuit. The switch in the circuit has remained in position 1 for a long time. At  $t = 0$ , the switch moves to the position 2. If  $R_s = 1000 \Omega$ ,  $R_f = 3000 \Omega$ ,  $R_g = 1000 \Omega$ ,  $R_i = 75 \text{ M}\Omega$ ,  $R_o = 50 \Omega$ ,  $A = 10^5$  and  $V_g = 10 \text{ V}$ . If  $\frac{V_0}{V_0 - 100} = \frac{-100t}{-100}$

- (a)  $V_0(t) = -60 + 90e^{-100t}$  for  $t \geq 0$
- (b)  $i_0(t) = -2.25e^{-100t}$  for  $t \geq 0^+$

$$c) (-2.25e-3) \left( \frac{d}{dt} [-60 + 90 e^{-100t}] \right)$$

$$(-2.25e-3)(-9000e^{-100t}) = (-2.25e-3)e^{-100t}$$

assuming  $i_0 = 2.25e^{-100t} \text{ mA}$

$$V_0(0) = 30$$

$$90e^{-100t} - 90 + 30$$

$$90e^{-100t} = 60$$

Check the consistency of the solutions (for  $V_0(t)$  and  $i_0(t)$ ) by deriving  $V_0(t)$  from  $i_0(t)$ .

(t) Lauren Yao and Koby Dunn have been best friends since middle school. However, a recent argument about a circuit problem has put a strain on their friendship. The bone of contention is as follows:

### Resistor

An A.C. voltage impressed across a pure resistance (or any other) in parallel with a pure inductance


### Resistor

An A.C. voltage impressed across a pure resistance of 3.5 Ohms in parallel with a pure inductance of impedance of 3.5 Ohms. The weight of the current (i.e., value of current is one component relative to the other) in the aforementioned passive components is in question.

If the current through the pure resistance and inductance are denoted as  $I_R$  and  $I_L$ , respectively.

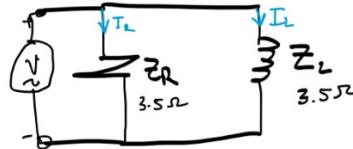- (i) Lauren claims that  $I_R > I_L$
- (ii) Koby claims that  $I_R < I_L$
- (iii) Roger (paper vendor down their street) claims that  $I_R = I_L$
- (iv) Mr Johnson (their neighbor) claims that none of the above answers are correct.

Help settle the dispute by stating the right answer.



Let the voltage across the pure resistor be

$$V_R = A \cos(\omega t) \text{ where } A \text{ is the Amplitude of Sine wave}$$

$$V = IR \Rightarrow I_R = \frac{A}{Z_R} \cos(\omega t) = \frac{1}{3.5} A \cos(\omega t)$$

(i) The current across an inductor w/ a AC volt is  $90^\circ$  out-of-phase from its voltage.

$$V_L \text{ is } V_R \text{ because of parallel} \Rightarrow V_L = A \cos(\omega t)$$

$$V = IR \Rightarrow I_L = \frac{A}{3.5} \cos(\omega t + 90^\circ)$$



\*  $90^\circ$  offset

$\Rightarrow$  Mr. Johnson is Right

Since both currents are greater than the other at different times.

Precisely, they are greater / less than one another  $1/2$  the time.

**Problem 2a.** The parameters for the circuit shown in Fig. 2 are  $R_a = 100\ \text{K}\Omega$ ,  $R_1 = 500\ \text{K}\Omega$ ,  $C_1 = 0.1\ \mu\text{F}$ ,  $R_b = 25\ \text{K}\Omega$ ,  $R_s = 100\ \text{K}\Omega$  and  $C_2 = 1\ \mu\text{F}$ . The power supply voltage for each op amp is  $\pm 6\text{V}$ . The

Ac couple  
Caps -  
inductor

**Problem 2a.** The parameters for the circuit shown in Fig. 2 are  $R_a = 100 \text{ k}\Omega$ ,  $R_1 = 500 \text{ k}\Omega$ ,  $C_1 = 0.1 \mu\text{F}$ ,  $R_b = 25 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$  and  $C_2 = 1 \mu\text{F}$ . The power supply voltage for each op amp is  $\pm 6\text{V}$ . The signal voltage ( $V_g$ ) for the cascaded integrating amplifiers jumps from 0 to  $250 \text{ mV}$  at  $t = 0$ . No energy is stored in the feedback capacitors at the instant the signal is applied.

- Derive an algebraic expression for the output voltage  $V_0$  as a function of the input voltage  $V_g$ .
- Derive the characteristic equation and solve for its roots.
- Find the numerical expression of the differential equation for  $V_0$ .
- Find  $V_0(t)$  for  $t \geq 0$ .
- Find the numerical expression of the differential equation for  $V_{01}$ .
- Find  $V_{01}(t)$  for  $t \geq 0$ .  $i = C \frac{dV}{dt}$

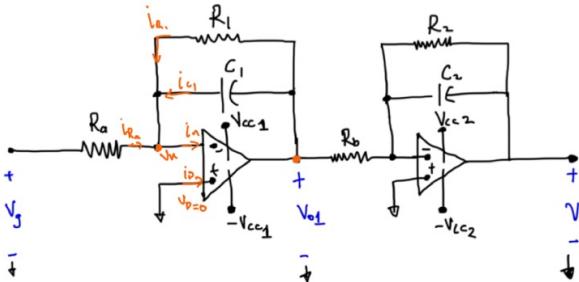


Fig. 2. Cascaded Integrating Amplifiers with RC Feedback Link.

$$\frac{kC_1}{R_a} @ V_n \\ i_g - i_n - i_{c1} - i_{c2} = 0$$

$$\frac{V_g - V_n}{R_a} - 0 - \frac{(V_n - V_{01})}{j\omega C_1} - \frac{(V_n - V_{01})}{R_1} = 0$$

$$V_n = V_p = 0$$

$$\frac{V_g}{R_a} = -\frac{V_{01}}{j\omega C_1} - \frac{V_{01}}{R_1} \quad * \\ = -\left(j\omega C_1 + \frac{1}{R_1}\right) V_{01}$$

$$\frac{V_g}{R_a} = -\left(\frac{j\omega C_1 R_1 + 1}{R_1}\right) V_{01}$$

$$\left( \frac{R_1}{R_a (j\omega C_1 R_1 + 1)} \right) V_g = V_{01} \quad *$$

Do same for  $V_0$

$$V_0 = H(s) V_g \\ V_g = \begin{cases} 0 & t < 0 \\ 250 \text{ mV} & t \geq 0 \end{cases} = V(t)$$

$$V_0 = H(s) \int \{ V(t) \} \quad *$$

$$V_0 \Rightarrow \frac{-25}{s} H(s) \quad \text{expand}$$

$$(iii) \quad H(s) = \left( \frac{-25 R_1 R_2}{R_a R_b (s)(sC_1 R_1 + 1)(sC_2 R_2 + 1)} \right) \text{ in Laplace Domain}$$

→ take the inverse Laplace of  $V_0(s)$  to determine  $V_0$  in time-domain

$$\int \{ V_0(s) \} = \int \{ \frac{-25 R_1 R_2}{R_a R_b (s)(sC_1 R_1 + 1)(sC_2 R_2 + 1)} \}$$

$$V_0(s) = \frac{-25 R_1 R_2}{R_a R_b} \int \{ \frac{1}{(s)(sC_1 R_1 + 1)(sC_2 R_2 + 1)} \}$$

$$\frac{1}{s(sC_1 R_1 + 1)(sC_2 R_2 + 1)} = \frac{A}{s} + \frac{B}{sC_1 R_1 + 1} + \frac{D}{sC_2 R_2 + 1}$$

$$\frac{V_0}{R_B} = -\left(\frac{j\omega C_1 R_1 + 1}{R_1}\right) V_{o1}$$

$$\left(-\frac{R_1}{R_B(j\omega C_1 R_1 + 1)}\right) V_{o1} = V_{o1} \quad \text{X}$$

Do same for  $V_o$

$$V_o = -\left(\frac{R_2}{R_B(j\omega C_2 R_2 + 1)}\right) V_{o2} \quad \text{X}$$

$$i) V_o = \left( \frac{R_1 R_2}{R_B R_B (j\omega C_1 R_1 + 1) (j\omega C_2 R_2 + 1)} \right) V_{o2}$$

Characteristic eqn for  $V_o$

$$\text{Let } k = \frac{R_1 R_2}{R_B R_B} \underline{V_{o2}}$$

$$\Rightarrow V_o = \frac{k}{(j\omega C_1 R_1 + 1)(j\omega C_2 R_2 + 1)}$$

Convert to S domain

$$V_o(s) = \frac{k}{(C_1 R_1 + 1)(C_2 R_2 + 1)} \leftarrow$$

Characteristic equation:

$$s^2 C_1 C_2 R_1 R_2 + C_1 R_1 + C_2 R_2 + 1 = 0 \quad \text{X}$$

$$(ii) s^2 C_1 C_2 R_1 R_2 + s(C_1 R_1 + C_2 R_2) + 1 = 0$$

$$s^2 + s \left( \frac{C_1 R_1 + C_2 R_2}{C_1 R_1 C_2 R_2} \right) + \frac{1}{C_1 R_1 C_2 R_2} = 0$$

$$s = \frac{-C_1 R_1 - C_2 R_2}{C_1 R_1 C_2 R_2} \pm \sqrt{\left(\frac{C_1 R_1 + C_2 R_2}{C_1 R_1 C_2 R_2}\right)^2 - \frac{4}{C_1 R_1 C_2 R_2}}$$

$$s = -15 \pm \frac{1}{2} \sqrt{30^2 - 800}$$

$$-15 \pm \frac{1}{2}(10) \Rightarrow \boxed{s_1 = -10} \\ \boxed{s_2 = -20}$$

$$V_{o1}(s) = H(s) \int \underline{V_{o2}(s)}$$

$$V_{o1}(s) = \left( \frac{-R_1}{R_B(C_1 R_1 + 1)} \right) \left( \frac{-25}{s} \right)$$

$$\int \underline{V_o(s)} = \int \left\{ \frac{.25 R_1 R_2}{R_A R_B (s(C_1 R_1 + 1)(C_2 R_2 + 1))} \right\}$$

$$V_o(s) = \frac{.25 R_1 R_2}{R_A R_B} \int \left\{ \frac{1}{(s(C_1 R_1 + 1)(C_2 R_2 + 1))} \right\}$$

$$\frac{1}{s(C_1 R_1 + 1)(C_2 R_2 + 1)} = \frac{A}{s} + \frac{B}{s(C_1 R_1 + 1)} + \frac{D}{s(C_2 R_2 + 1)}$$

$$\Rightarrow \frac{A}{s} + \frac{B}{s(C_1 R_1 + 1)} + \frac{D}{s(C_2 R_2 + 1)}$$

via Partial fraction decomposition

$$\Rightarrow \int \frac{1}{s} + \frac{1}{s+20} + \frac{-2}{s+10} \quad \text{3}$$

$$V_o(t) = 5 \left[ 1 + e^{-20t} - 2e^{-10t} \right]$$

$$\boxed{(iv) V_o(t) = 5 + 5e^{-20t} - 10e^{-10t}}$$

Characteristic equation:

$$S^2 C_1 C_2 R_1 R_2 + S C_1 R_1 + S C_2 R_2 + 1 = 0$$

(ii)  $S^2 C_1 C_2 R_1 R_2 + S(C_1 R_1 + C_2 R_2) + 1 = 0$

$$S^2 + S \left( \frac{C_1 R_1 + C_2 R_2}{C_1 R_1 C_2 R_2} \right) + \frac{1}{C_1 R_1 C_2 R_2} = 0$$

$$S = \frac{-\frac{C_1 R_1 + C_2 R_2}{C_1 R_1 C_2 R_2} \pm \sqrt{\left(\frac{C_1 R_1 + C_2 R_2}{C_1 R_1 C_2 R_2}\right)^2 - \frac{4}{C_1 R_1 C_2 R_2}}}{2}$$

$$S = -15 \pm \frac{1}{2} \sqrt{30^2 - 800}$$
$$-15 \pm \frac{1}{2}(10) \Rightarrow \begin{cases} S_1 = -10 \\ S_2 = -20 \end{cases}$$

$$V_{o1}(s) = H(s) \sum V_g(t)$$

$$V_{o1}(s) = \left( \frac{-R_1}{R_a (S C_1 R_1 + 1)} \right) \left( \frac{25}{s} \right)$$

(V)  $V_{o1}(s) = -\frac{25 R_1}{R_a} \left( \frac{1}{S C_1 R_1 + 1} \right)$

$$\frac{A}{s} + \frac{B}{s+0.05} = \frac{1}{s(s+0.05+1)}$$
$$A(s+0.05+1) + B(s) = 1 \quad \text{for } s=0$$
$$A=1$$

$$s = -20$$
$$B = -1/20$$

$$\int^{-1} \{V_{o1}(s)\} = -\frac{25 R_1}{R_a} \int^{-1} \left\{ \frac{1}{s(s+0.05+1)} \right\}$$

$$V_{o1}(t) = -\frac{25 R_1}{R_a} \left[ \int^{-1} \left\{ \frac{1}{s} \right\} - \frac{1}{20} \int^{-1} \left\{ \frac{1}{s+0.05+1} \right\} \right]$$

$$-\frac{25 R_1}{R_a} \left[ 1 - \int^{-1} \left\{ \frac{1}{s+20} \right\} \right]$$

$$\frac{-25 R_1}{R_a} \left[ 1 - e^{-20t} \right] =: 1.25 e^{-20t} - 1.25 = V_{o1}(t) \quad (\text{VI})$$

**Problem 2b.** Repeat Problem 2a with the feedback resistors  $R_1$  and  $R_2$  removed.

VCL @ V<sub>n</sub> is Reduced

$$\frac{V_g}{R_a} = \frac{-V_{o1}}{1/SC_1}$$

$$\frac{V_g}{R_a} = -V_{o1}(SC_1)$$

$$\Rightarrow V_{o1} = \frac{-1}{R_a(SC_1)} V_g \quad \text{X}$$

$$V_o = \frac{-1}{R_b(SC_2)} V_{o1} \Rightarrow$$

$$V_o = \left( \frac{1}{R_a(SC_1)} \right) \left( \frac{1}{R_b(SC_2)} \right) V_g$$

(i)  $\boxed{V_o = \frac{1}{R_a R_b S^2 C_1 C_2} V_g}$

Transfer Function: let

$$k = \frac{1}{R_a R_b C_1 C_2}$$

$$H(s) = \frac{k}{s^2}$$

(ii)  $s^2 = 0$

$$s = 0$$

$$V_o = H(s) V_g(s) \quad V_g(s) = \int \sum V_g(t) \quad \text{?}$$

$$V_o(s) = .25 H(s) \left( \frac{1}{s} \right) \quad \Rightarrow \quad \frac{.25}{s}$$

(iii)  $\boxed{V_o(s) = \frac{.25}{R_a R_b S^2 C_1 C_2}}$

$$\int \sum V_o(s) = \frac{.25}{R_a R_b C_1 C_2} \left( \frac{1}{s} \right) \sum \frac{1}{s^3}$$

(iv)  $\boxed{V_o(t) = \begin{cases} 500 t^2 & 0 \leq t \leq 10^{-5} \\ 6 & t \geq 10^{-5} \end{cases}}$

(v)  $V_{o1} = \frac{-1}{R_a C_1 S} \left( \frac{.25}{s} \right) \Rightarrow \left( \frac{.25}{R_a C_1} \right) \frac{1}{s^2} = V_o(s)$

(vi)  $\boxed{V_{o1}(t) = \frac{25}{.01} t \Rightarrow -25t \Rightarrow \begin{cases} -25t & 0 \leq t \leq 2.7 \\ -6 & t \geq 2.7 \end{cases}}$

**Problem 3.** The *n*-type metal oxide semiconductor (MOSFET) transistor (see Fig. 3) is a three-terminal component that serves as a building block for almost all digital electronic devices.

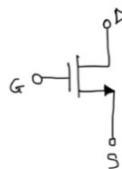


Fig. 3. MOSFET (NMOS) with terminals labeled as Gate (G), Source (S) and Drain (D)

The *n*-type MOSFET (NMOS) has two operation modes namely (i) triode mode, and (ii) saturation mode i.e., active mode. A large scale equivalent circuit model for the NMOS in the saturation mode is shown in Fig. 4.

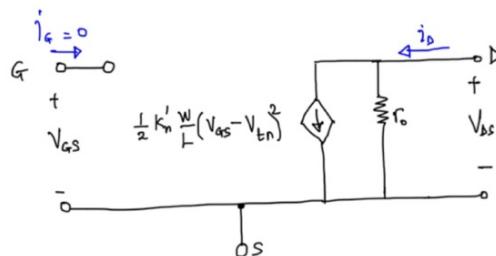



Fig. 4. Large-signal equivalent circuit model of the *n*-channel MOSFET in saturation.

In the circuit above,  $r_0 \approx \left[ \frac{di_D}{dv_{DS}} \right]_{V_{GS}=\text{constant}}$  while the drain current  $i_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{tn})^2$ .

There are rules guiding the operation of an NMOS transistor.

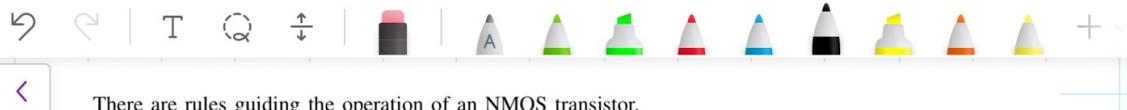- (i) **RULE 1:** The NMOS will operate in the saturation (active) mode if the drain voltage ( $V_D$ ) is greater than the difference between the gate voltage ( $V_G$ ) and the threshold voltage ( $V_{tn}$ ) i.e.  $V_D > V_G - V_{tn}$ .
- (ii) **RULE 2:** The source voltage ( $V_S$ ) must not exceed the gate voltage ( $V_G$ ). A situation where  $V_S > V_G$  implies that the transistor is inactive i.e., cut off.

Using the rules stated above, analyze the active circuit shown in Fig. 5(b) – annotated version of Fig. 5(a). Find the voltages ( $V_S$ ,  $V_D$ ,  $V_{GS}$ ) at all nodes and the current  $i_D$ . Let  $V_{tn} = 1$  V,  $i_G = 0$  A, and  $k_n(W/L) = 1$  mA/V<sup>2</sup>.



Using the rules stated above, analyze the active circuit shown in Fig. 5(b) – annotated version of Fig. 5(a). Find the voltages ( $V_S$ ,  $V_D$ ,  $V_{GS}$ ) at all nodes and the current  $i_D$ . Let  $V_{th} = 1$  V,  $i_G = 0$  A, and  $k_n(W/L) = 1 \text{ mA/V}^2$ .

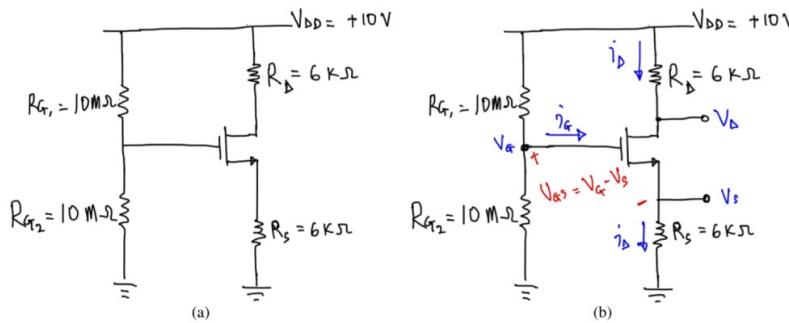


Fig. 5. (a) Original circuit (b) circuit with additional details

$$V_S = i_D \cdot R_S \Rightarrow i_D (6k) = i_D \cdot 6 \Rightarrow 6A$$

$$V_g = 5V \text{ due to } R_{G1} + R_{G2} \text{ being}$$

Since  $\Rightarrow$  voltage divider directly in half

$$V_{GS} = 5 - i_D R_S \Rightarrow 5 - i_D (6)$$

$$\begin{aligned} i_D &= \frac{1}{2} k' \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 \\ &\Rightarrow \frac{1}{2} (1) (5 - i_D (6) - 1)^2 \end{aligned}$$

$$i_D = \frac{1}{2} (1) (4 - 6 i_D)^2$$



&lt;

$$i_D = \frac{1}{2} k' \left(\frac{w}{L}\right) (V_{DS} - V_{TN})^2$$

$$\Rightarrow \frac{1}{2} (1) (5 - i_D (6)^{-1})^2$$

$$i_D = \frac{1}{2} (1) (4 - 6 i_D)^2$$

$$i_D = \frac{1}{2} [16 - 48 i_D + 36 i_D^2]$$

$$18 i_D^2 - 24 i_D + 8 = 0$$

$$18 i_D^2 - 25 i_D + 8 = 0$$

$$i_D = .89 \text{ mA}$$

$$i_{D_2} = .5 \text{ mA}$$

$$V_S = i_D \cdot R_S$$

$$= (.89 \times 10^{-3})(6 \times 10^3) \Rightarrow 5.34 \text{ V} > 5$$

$$\Rightarrow V_S > V_D$$

which is NOT  
allowed  
Rule 2

$i_D = .5 \text{ mA}$

$V_S = 3 \text{ V}$


$V_D = 5 \text{ V}$

$V_{DS} = 2 \text{ V}$

$V_D = 10 - V_S = 7 \text{ V}$

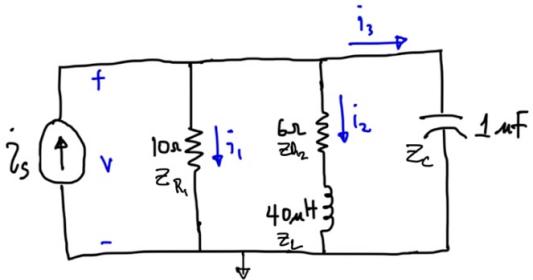**Problem 4a.** The sinusoidal current source in the circuit shown in Fig. 6 produces the current  $i_s = 8\cos(200000t)$  A.

- Construct the frequency-domain equivalent circuit.
- Find the steady-state expression for  $v$ ,  $i_1$ ,  $i_2$ , and  $i_3$ .



$$Z_C = \frac{1}{s(1e-6)} \quad Z_L = s(40e-6) \quad Z_{R1} = 10 \Omega \quad Z_{R2} = 6 \Omega$$


$$s = j\omega$$

convert  $\omega = 8 \cos(200,000 t)$  to frequency domain

$$A e^{j\phi} e^{j\omega t}$$

→ phasor form  
 $\phi = 0$

$$I = 8 e^{j0} \Rightarrow 8 A$$

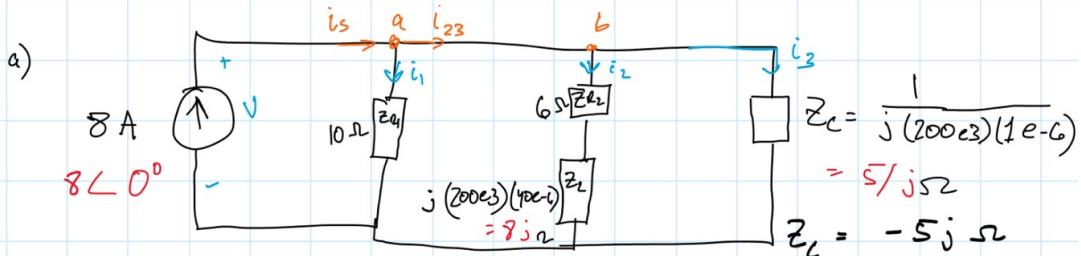

$$6 + 8j = Z_{R1}$$

$$\Rightarrow 10L .92729$$






&lt;

$$6 + 8j = Z_{RL}$$


$$\Rightarrow 10L e^{j92.729}$$

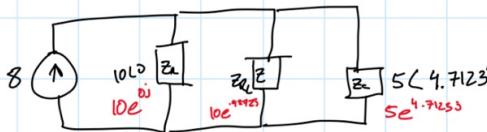

$$\left[ \frac{1}{10} + \frac{1}{10} e^{-j92.729} + \frac{1}{5} e^{-j4.7123} \right]^{-1}$$

$$(10) \left[ 1 + e^{-j92.729} + 2e^{-j4.7123} \right]^{-1}$$

$$= 5e^{-j0.6435} = Z_{eq}$$

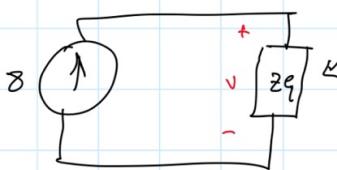

$$i_1 = \frac{v}{Z_{A1}}$$

$$V = I \cdot Z_{eq} \Rightarrow 8 \cdot 5 e^{-j0.6435}$$

$$i_2 = \frac{v}{(Z_{R2} + Z_0)}$$

$$i_3 = \frac{v}{Z_{C1}}$$

$$V \Rightarrow 40e^{-j0.6435} V \Rightarrow 40 \cos(200,000t - 36.87) V$$

$$i_1 = 4e^{-j0.6435} A \Rightarrow 4 \cos(200,000t - 36.87) A$$

$$i_2 = 4e^{-j1.5708} A \Rightarrow 4 \cos(200,000t - 90) A$$

$$i_3 = 8e^{-j92.729} A \Rightarrow 8 \cos(200,000t + 53.13) A$$



T



10

**Problem 4b.** For the circuit shown in Fig. 7, find:

- The value of  $R_L$  that results in maximum power being transferred to  $R_L$
- Calculate the maximum power that can be delivered to  $R_L$
- When  $R_L$  is adjusted for maximum power transfer, what percentage of the power delivered by the 360 V source reaches  $R_L$ ?

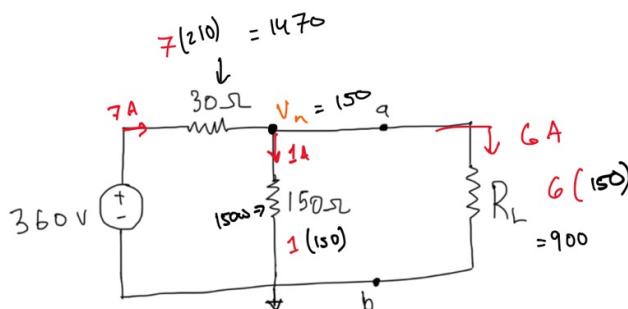


Fig. 7. RLC Network with sinusoidal current source

(i) Maximum Power Transfer Theorem States  
TO DELIVER MAX POWER,  $R_L = R_{Th}$   
 $\Rightarrow R_L = 25 \Omega$   
Given That  $R_L = 25 \Omega$

$V_{Th} \Rightarrow$ 
 $= \frac{150}{180}(300) = 300$

$P_{max} = \frac{V_{Th}^2}{R_{Th}} = 1900 \text{ watts}$

$P_{30\Omega} = \frac{V^2}{R} = \frac{210^2}{30} = 1470 \text{ watts}$

$P_{150\Omega} = \frac{V^2}{R} = \frac{150^2}{150} = 150 \text{ watts}$


$P_{R_L} = \frac{150^2}{25} = 900 \text{ watts}$

$\Rightarrow 35.71\% \text{ of } 360 \text{ V source}$



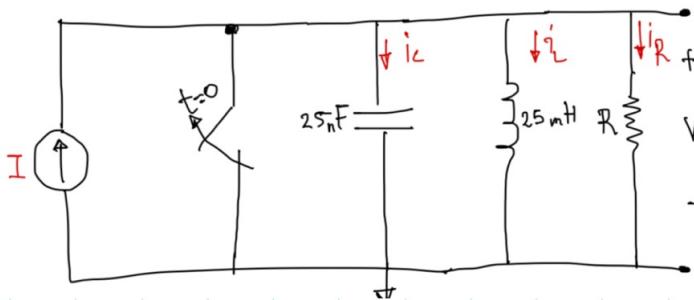**Problem 5a.** The initial energy stored in the circuit in Fig. 8 is zero. At  $t = 0$ , a dc current source of 24 mA is applied to the circuit. The value of the resistor is  $400 \Omega$ .

- What is the initial value of  $i_L$ ?
- What is the initial value of  $di_L/dt$ ?
- What are the roots of the characteristic equation?
- What is the numerical expression for  $i_L(t)$  when  $t \geq 0$ ?
- Find  $i_L(t)$  for  $t \geq 0$  if the resistor  $R$  in Fig. 8 is increased to  $625 \Omega$ .
- Find  $i_L(t)$  for  $t \geq 0$  if the resistor  $R$  in Fig. 8 is increased to  $500 \Omega$ .



a) Since there is no energy in circuit for  $t < 0$   
 $i_L$  at  $t = 0$  will be zero

$$i_L(0) = 0$$

b) Given that there is no energy in the capacitor at  $t = 0$ .  
Then voltage across it is zero.

$\Rightarrow$  voltage across inductor is also zero

$$V = L \frac{di}{dt} \Rightarrow 0 = L \frac{di}{dt} \Rightarrow \boxed{\frac{di_L}{dt} = 0}$$

c)

$$\boxed{\left[ S^2 + \frac{1}{RC} + \frac{1}{LC} \right] = 0}$$

↓  
this is the  
characteristic Eqn

$$S_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$S_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$



5 | T | Q |  $\frac{1}{\cdot}$  |



c)

$$\left[ s^2 + \frac{s}{RC} + \frac{1}{LC} \right] = 0$$

↓  
this is the  
characteristic Eqn

$$S_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$S_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$S_1 = \frac{-1}{2(400)(25e-9)} - \sqrt{\left[\frac{1}{2(400)(25e-9)}\right]^2 - \frac{1}{(25e-3)(25e-9)}}$$

$$= -80,000$$

$$S_2 = -\frac{1}{2(400)(25e-9)} + \sqrt{\left[\frac{1}{2(400)(25e-9)}\right]^2 - \frac{1}{(25e-3)(25e-9)}}$$

$$= 20,000$$

D) Since The Radian frequency squared is less than Damping frequency squared  $\Rightarrow$  overamped inductor

$$i_L = I_f + A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$\frac{d i_L}{dt} = A_1 S_1 e^{S_1 t} + A_2 S_2 e^{S_2 t}$$

Take a @  $t=0$

$$I_f + A_1 + A_2 = 0 \Rightarrow$$

$$A_1 S_1 + A_2 S_2 = 0 \Rightarrow$$

$$\begin{bmatrix} -80e3 & -20e3 & 0 \\ 1 & 1 & 1 \\ 1 & 1 & -0.02 \end{bmatrix}$$

$$\Rightarrow -0.032 + .008$$

$$i_L = .024 - .032 e^{-20000t} + .008 e^{80000t}$$

5 | T Q ↴ | A | A | A | A | A | A | A | A | +

D) Since The Radian frequency squared is less than Damping frequency squared  $\Rightarrow$  overdamped inductor

$$i_L = I_f + A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$\frac{di_L}{dt} = A_1 S_1 e^{S_1 t} + A_2 S_2 e^{S_2 t}$$

Take at  $t=0$

$$I_f + A_1 + A_2 = 0 \Rightarrow$$

$$A_1 S_1 + A_2 S_2 = 0 \Rightarrow$$

$$\begin{bmatrix} -80e3 & -20e3 & 0 \\ 1 & 1 & -0.02 \end{bmatrix}$$

$$\Rightarrow -0.032 + .008$$

$$i_L = .024 - .032 e^{-20000t} + .008 e^{-80000t}$$

c) if  $R$  is increased to  $625 \Omega$

$$s = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \Rightarrow -3.2e4 \pm j2.4e4$$

$$\omega = \frac{1}{LC} \quad \alpha = \frac{1}{2RC}$$

$$\omega_0 = 1.6e9 \quad \alpha = 32e3$$

$\omega_0^2 > \alpha^2 \Rightarrow$  roots turn complex + The system is underdamped

$$\Rightarrow i_L = I_f + B_1 e^{S_1 t} \cos(\omega_0 t) + B_2 e^{S_2 t} \sin(\omega_0 t)$$

$$\text{at } t=0 \Rightarrow 0 = I_f + B_1(1)(1) + \cancel{B_2(1)(0)} \Rightarrow 0$$

$$\Rightarrow B_1 = -I_f \Rightarrow -0.024$$

$$\frac{di_L}{dt} = B_1 \left( -\omega_0 \sin(\omega_0 t) e^{-\alpha t} + \alpha e^{-\alpha t} \cos(\omega_0 t) \right) +$$

$$B_2 \left( \omega_0 \cos(\omega_0 t) \dot{e}^{-\alpha t} + \omega_0 \frac{\alpha}{\omega_0} e^{-\alpha t} \sin(\omega_0 t) \right) \Big|_{t=0}$$

$$\frac{di_L(0)}{dt} = -B_1 + \omega_0 B_2 = 0$$

$$\frac{-0.024(S_1)}{\omega_0} = B_2 = .032$$

$$i_L(t) = .024 - .024 e^{-32e3t} \cos(24000t) - .032 e^{-32e3t} \sin(24000t)$$

| T  $\frac{d}{dt}$  | A + <

$$\omega_0 = 1.6 \text{ e9} \quad \alpha = 32 \text{ e3}$$

$\omega_0^2 > \alpha^2 \Rightarrow$  Roots turn complex + the system is underdamped

$$\Rightarrow i_L = I_f + B_1 e^{st} \cos(\omega_0 t) + B_2 e^{st} \sin(\omega_0 t)$$

$$\text{At } t=0 \Rightarrow 0 = I_f + B_1(1) + \cancel{B_2(1)} \Rightarrow 0 \\ \Rightarrow B_1 = -I_f \Rightarrow -0.024$$

$$\frac{di_L}{dt} = B_1 \left( \cancel{-\omega_0 \sin(\omega_0 t)} e^{-\alpha t} + \cancel{-\alpha e^{-\alpha t} \cos(\omega_0 t)} \right) + \\ B_2 \left( \omega_0 \cancel{\cos(\omega_0 t)} e^{-\alpha t} + \cancel{\omega_0^2 e^{-\alpha t} \sin(\omega_0 t)} \right) \Big|_{t=0}$$

$$\frac{di_L(0)}{dt} = -B_1 + \omega_0 B_2 = 0 \\ \frac{-0.024(s)}{\omega_0} = B_2 = -0.032$$

$$i_L(t) = .024 - .024 e^{-22e3t} \cos(24000t) - .032 e^{-22e3t} \sin(24000t)$$

f) Given  $R = 500$

$$S = \frac{1}{2RC} \pm \sqrt{\left[ \frac{1}{2RC} \right]^2 - \frac{1}{LC}} \Rightarrow S = \frac{1}{2RC} = 40,000$$

is such that  $\omega_0^2 = \alpha^2$

Resulting in a repeated root

$$\Rightarrow i_L = I_f + A_1 t e^{st} + A_2 e^{st}$$

$$\text{At } t=0 \Rightarrow A_2 = -I_f = -.024$$

$$\frac{di_L}{dt} = A_1 (t(s)e^{st} + e^{st}) + A_2 s e^{st}$$

$$\frac{di_L(0)}{dt} = A_1 + A_2 s = 0$$

$$A_1 = -A_2 s \Rightarrow .024(40,000) = 960$$


$$i_L = .024 + 960 t e^{40000t} + -.024 e^{40000t}$$



**Problem 5b.** Energy is stored in the circuit in Fig. 8 at the instant the dc current source is applied. If the resistance is  $R = 500 \Omega$  and initial current in the inductor is  $29 \text{ mA}$  with the initial voltage across the capacitor being  $50 \text{ V}$ . Find

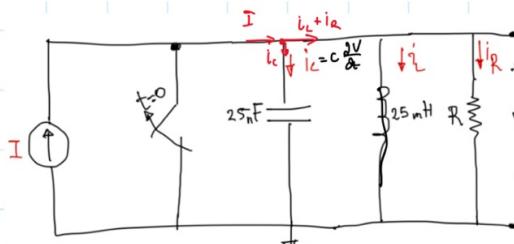- (i)  $i_L(0)$
- (ii)  $\frac{di_L(0)}{dt}$
- (iii)  $i_L(t)$  for  $t \geq 0$
- (iv)  $v(t)$  for  $t \geq 0^+$ .

$$\begin{aligned} V_L &= L \frac{di}{dt} & (i) i_L(0) &= \boxed{0.029 \text{ A}} \\ && (ii) v_L &= (25 \text{ e-3}) \frac{di_L(0)}{dt} \\ && &\Rightarrow \frac{50}{25 \text{ e-3}} = \boxed{2000 \text{ A/s}} \end{aligned}$$



$$I - i_C - (i_L + i_R) = 0$$

$$0.029 - C \frac{dv}{dt} - i_L(t) - \frac{v(t)}{R} = 0$$

$$\text{Given that } V_L = L \frac{di_L}{dt}$$

$$V_L = V_C = V_R = V$$

$$\frac{dv}{dt} = L \frac{d^2 i_L}{dt^2}$$

$$-CL \frac{d^2 i_L}{dt^2} - \frac{L}{R} \frac{di_L}{dt} - i_L + 0.029 = 0$$

$$LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = 0.029$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{0.029}{LC}$$

$$\text{Let } i_L = e^{\alpha t} \Rightarrow \frac{di_L}{dt} = \alpha e^{\alpha t} \dots \quad \text{first solve}$$

$$d^2 e^{\alpha t} + \frac{1}{LC} \alpha e^{\alpha t} + \frac{1}{LC} e^{\alpha t} = 0 \quad \text{the homogeneous solution}$$

$$\alpha^2 + \frac{1}{RC} \alpha + \frac{1}{LC} = 0$$

$$\alpha^2 + \frac{1}{RC} \alpha + \frac{1}{LC} = 0$$

$$\alpha = -\frac{1}{2RC} \pm \frac{1}{2} \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

$$= -40000 \pm 0$$

$$\text{form } i_{Lp}(t) = A_1 e^{-40000t} + A_2 e^{-40000t} + i_{LP}$$

$$i_L(0) = 0.029 = A_2 + i_{LP} \quad A_2 = 0.005$$

$$\frac{d i_L(t)}{dt} = A_1 (e^{-40000t} + t(-40000) e^{-40000t}) + A_2 (-40000) e^{-40000t}$$



$$\text{Let } i_L = e^{\alpha t} \Rightarrow \frac{di_L}{dt} = \alpha e^{\alpha t} \dots \text{ first solve}$$

$$d^2 e^{\alpha t} + \frac{1}{LC} \alpha e^{\alpha t} + \frac{1}{LC} e^{\alpha t} = 0^2 \quad \text{The homogeneous solution}$$

$$\alpha^2 + \frac{1}{LC} \alpha + \frac{1}{LC} = 0$$

$$\alpha^2 + \frac{1}{LC} \alpha + \frac{1}{LC} = 0$$

$$\alpha = -\frac{1}{2LC} \pm \frac{1}{2} \sqrt{[Y_{RC}]^2 - \frac{4}{LC}}$$

$$= -40000 \pm 0$$

$$\text{General } i_{L_0}(t) = A_1 e^{-40000t} + A_2 e^{-40000t} + i_{LP}$$

$$i_L(0) = .024 = A_2 + i_{LP} \quad A_2 = .005$$

$$\frac{d i_L(t)}{dt} = A_1 (-40000e^{-40000t}) + t(-40000)(-40000e^{-40000t}) + A_2 (-40000)e^{-40000t}$$

$$\frac{d i_L(0)}{dt} = A_1 + A_2 (-40000) = 2000$$

$$A_1 + 2000 = 2000$$

$$A_1 = 2000$$

(iii)  $i_L(t) = .024 + 2000t e^{-40000t} + .005 e^{-40000t}$

$$(IV) L \frac{di_L(t)}{dt} = V_L \Rightarrow$$

$$V_L(t) = (25C - 3)(2200(-40000)t e^{-40000t} + 2200 e^{-40000t} - 200 e^{-40000t})$$

$$\boxed{V(t) = (-2.2e6)t e^{-40000t} + 50 e^{-40000t}}$$