

Q1 According to the scaling model proposed by Dennard *et al.*, in every subsequent generation, all three physical dimensions (W, L, t_{ox}), the power supply voltage V_{DD} and the threshold voltage, V_t are downscaled by factor of x ($x > 1$). Show that in this scenario, the clock frequency can be increased by a factor of x while keeping the chip power density (in W/cm^2) keeping the same. [25 pts]

The chip power density is a function of Area A . The # of transistors N for generation n (N_n) is $N_n = \frac{A}{w_n l_n}$

for $N_{n+1} = \frac{A}{(w/x)(l/x)} \Rightarrow N_n x^2$

The delay $T_n = \frac{C l_n V_{DDn}}{I_{on,n}}$ scales by x

as $I_{on(n+1)} = \frac{I_{on,n}}{x}$ and $l_{n+1} = \frac{l_n}{x} \Rightarrow t_{n+1} = \frac{t_n}{x}$

$$f_n = \frac{1}{T_n} \quad f_{n+1} = \frac{1}{t_{n+1}} = \frac{1}{t_n/x} = \frac{x}{t_n} = \underline{f_n x}$$

if we see that the chip Power, $n = C l_n V_{DD}^2 f_n$

* scaling f_{n+1} by x

keeps the power density constant.

$$P_{n+1} = C \frac{l_n}{x} \frac{V_{DD}^2}{x^2} f_n x$$

$$P_{n+1} = P_n / x^2$$

$$\Rightarrow P_{chip} P_{n+1} = N_{n+1} P_{n+1}$$

$$P_{chip} P_{n+1} = N_n \cancel{x^2} \frac{P_n}{\cancel{x^2}}$$

Q2 In the scenario where, in each subsequent generation, you could downscale only the three physical dimensions (W, L, t_{ox}) by a factor of x but had to keep V_{DD} and V_t fixed, how would you have changed the clock frequency?
[25 pts]

Beav's - The # of transistors is dependent on Area and Physical Dimensions $W, L, t_{ox} \Rightarrow$ # of Transistors scales by x^2 still.

Capacitance also scales by $1/x$

$$P_{n+1} = \frac{C L_n}{x} V_{DD}^2 f_{n+1} = \left(\frac{P_n f_{n+1}}{f_n x} \right) N_n x^2$$


if Chip Power is constant $\Rightarrow x \frac{f_{n+1}}{f_n} = 1 \Rightarrow$

$$\boxed{f_{n+1} = \frac{f_n}{x}}$$

Q3 Consider an inverter with its input voltage $V_{in} = 0$. Why would the inverter dissipate power even in this case? [15 pts]

Leakage current!


@ $V_{in} = 0$

 

$$I_{off} = I_0 (V_{gsn} = 0, V_{dsn} = V_{DD})$$

$$P = V_{DD} \cdot I_{off}$$

 Q4 In an inverter, how will the power dissipated due to the short circuit current change if the inverter delay becomes larger? [20 pts]



Power is $= IV$ or $P = \int I dV$

if the delay is increased dramatically, π is

current switching would be non zero for longer as $I = \frac{dV}{dt} \Rightarrow$ longer delay implies

a larger average short circuit current. in π

case of MOS physics $P_{sc} = V_{DD} I_{avg} t_{sc}$

where t_{sc} is the short circuit duration.

$\uparrow t_p \Rightarrow \uparrow P_{dissipated}$

Q5 Consider an inverter operating at $V_{DD}=5$ V. For the following cases, determine whether $NM_L=NM_H$ or $NM_L>NM_H$ or $NM_L<NM_H$? Assume that both the NMOSFET and PMOSFET has the same t_{ox} and $\mu_n=3\mu_p$. The analysis requires calculation of the middle voltage V_M and comparison of the transfer curves for different cases. [15 pts]

[Q1.1] $W_p = W_n$, $V_{t,n}=|V_{t,p}|=1$ V.


[Q1.2] $W_p = 3 \times W_n$, $V_{t,n}=|V_{t,p}|=1$ V.

[Q1.3] $W_p = 3 \times W_n$, $V_{t,n}=1.5$ V, $|V_{t,p}|=0.5$ V.

Q5.1) Given that $\frac{P_D}{P_n} = \frac{\cancel{V_{P, Cox}} \cdot \cancel{\frac{W_p}{L_p}}}{\cancel{W_n} \cdot \cancel{\frac{L_n}{L_p}}} = \frac{V_p}{3V_n} = \frac{1}{3}$

$$\sqrt{\frac{P_D}{P_n}} = \sqrt{\frac{1}{3}}$$

$$V_n = \frac{\sqrt{\frac{P_D}{P_n}} (V_{DD} - |V_{t,p}|) + V_{t,n}}{1 + \sqrt{\frac{P_D}{P_n}}} \Rightarrow \frac{\sqrt{\frac{1}{3}} \cdot 5}{1 + \sqrt{\frac{1}{3}}} \approx 2.09 \text{ V}$$

 

$$Q5.2) \sqrt{\frac{\beta_p}{\beta_n}} = \sqrt{\frac{\frac{1}{2} \frac{C_{ox}}{C_{ox}} \frac{W_p}{L_p}}{\frac{W_n}{L_n}}} = \frac{\frac{1}{2} \frac{W_p}{L_p}}{\frac{W_n}{L_n}} = 1$$

$$(V_{tp}) = V_{tn} \quad \nabla$$

$$\text{for Perfect Ratio} \Rightarrow V_M = \frac{V_{DD}}{2}$$

$$\Rightarrow V_{TC} \text{ Ident} \Rightarrow \boxed{NM_H = NM_L}$$

Q5.3) Same widths as (5.3)

$$\Rightarrow V_M = \frac{(1)(5 - 0.5) + 1.5}{2} \Rightarrow 3V$$

