
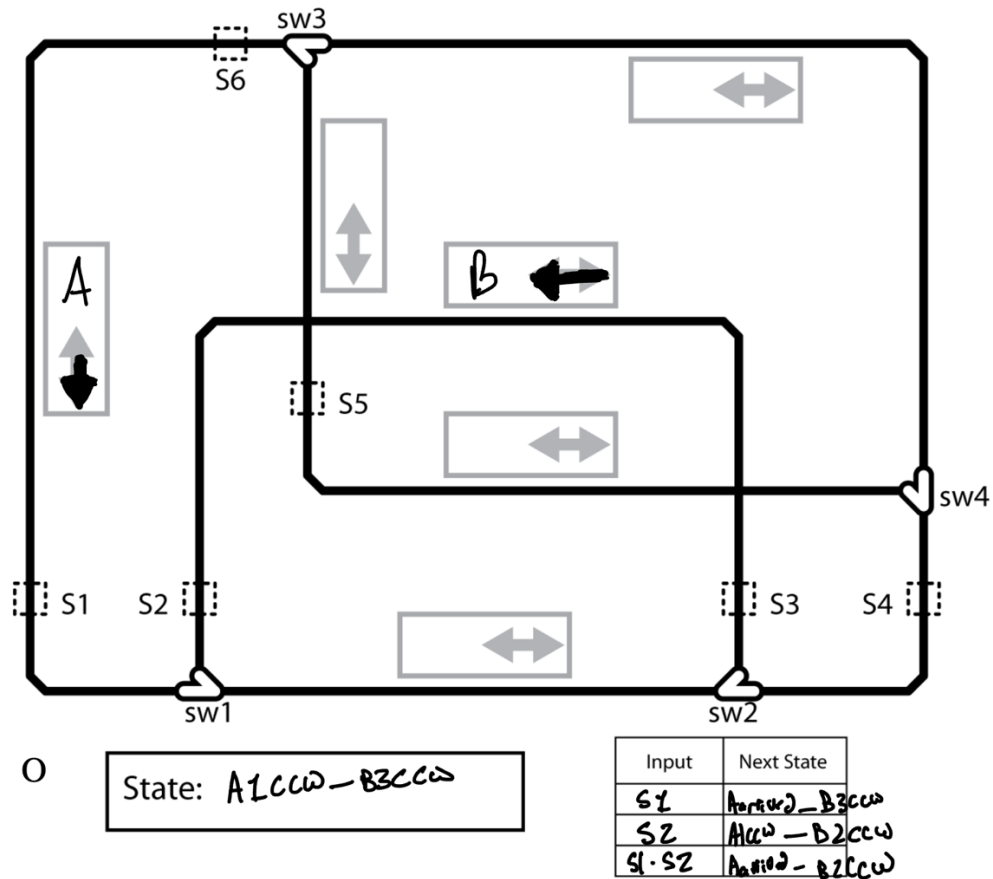



Rudra Goel  
Lab 06 Report  
ECE 2031 L10  
06 October 2024

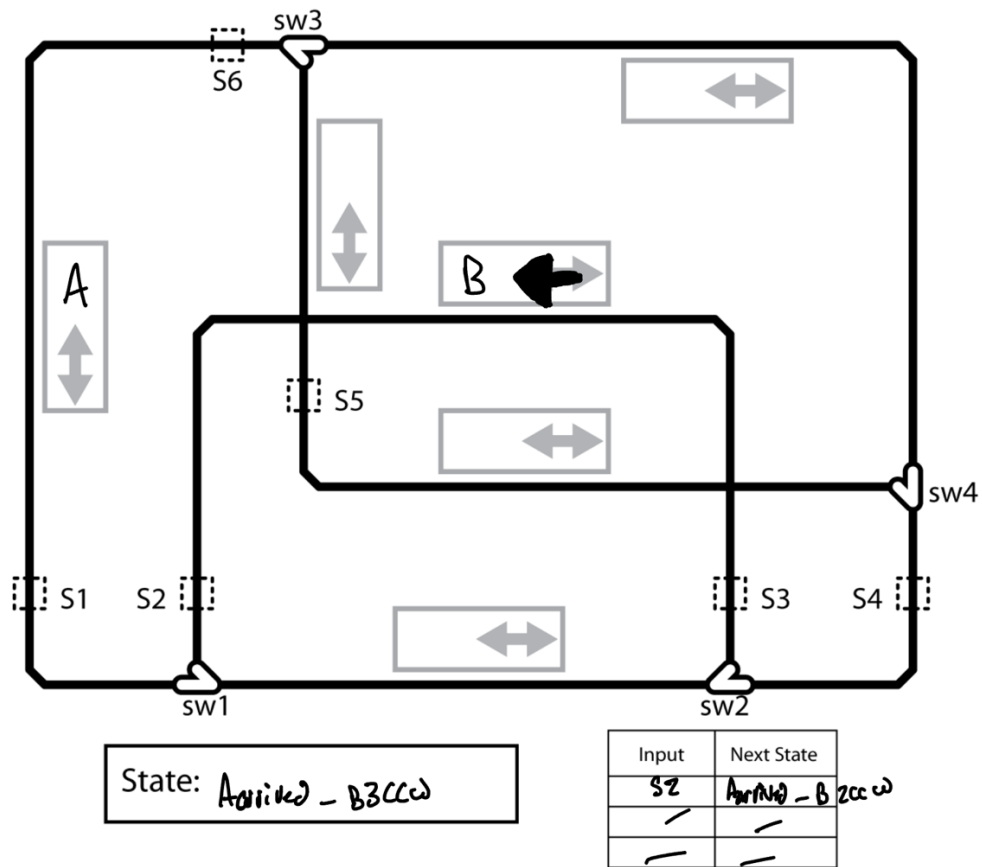


**Figure 1.** Worksheet diagram of state A1CCW\_B3CCW where Train A is on track 1 going counterclockwise, and Train B is on track 3 going counterclockwise. At this state, the switches do not need to be asserted to any logic level. When sensor 1 (S1) is asserted, state transitions to Aarrived\_B3CCW; when sensor 2 (S2) is asserted, state moves to A1CCW\_B2CCW; when both sensors are asserted ( $S1 \cdot S2$ ), state transitions to Aarrived\_B2CCW.




**Figure 2.** Worksheet diagram of state Aarrived\_B3CCW where Train A is stopped at sensor 1, and Train B is on track 3 going counterclockwise. At this state, the switches do not need to be asserted to any logic level. When sensor 2 (S2) is asserted, state moves to Aarrived\_B2CCW.

 


**Figure 3.** Worksheet diagram of state A1CCW\_B2CCW where Train A is on track 1 going counterclockwise, and Train B is on track 2 going counterclockwise. Switch 1 is asserted logic high to connect track 3 to track 2. Switch two is asserted logic low to keep track 2 connected with itself. When sensor 1 (S1) is asserted, state transitions to Aarrived\_B2CCW; when sensor 4 (S4) is asserted, state moves to A1CCW\_B2CW; when both sensors are asserted ( $S1 \cdot S4$ ), state transitions to Aarrived\_B2CW.

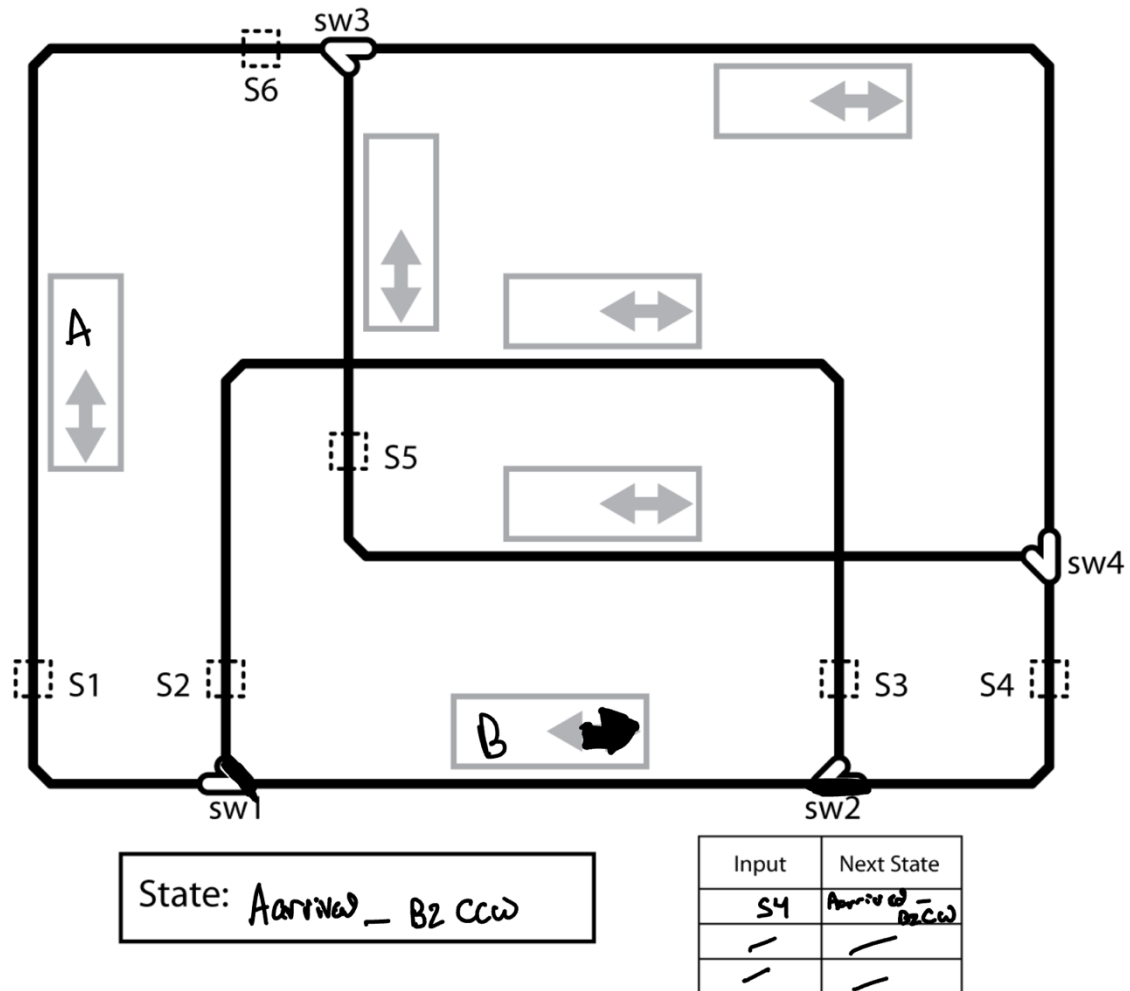

**Figure 4.** Worksheet diagram of state Aarrived\_B2CCW where Train A is stationary at sensor 1, and Train B is on track 2 going counterclockwise. Switch 1 is asserted logic high to connect track 3 to track 2. Switch 2 is asserted logic low to keep track 2 connected. When sensor 4 (S4) is asserted, state moves to A1CCW\_B2CW.

 


**Figure 5.** Worksheet diagram of state Aarrived\_B2CW where Train A is stationary at sensor 1, and Train B is on track 2 going counterclockwise. Switch 1 is asserted logic low to connect track 1 to track 2. Switch 2 is asserted logic low to keep track 2 connected with itself. There is no next state as this state is certain to crash the trains at sensor 1.

 

**Figure 6.** Worksheet diagram of state A1CCW\_B2CW where Train A is on track 1 going counterclockwise, and Train B is on track 2 going clockwise. At this state, switch 1 is asserted to logic high to connect track 3 to track 2. Switch 2 is asserted logic low to keep track 2 connected with itself. When sensor 1 (S1) is asserted, state transitions to Arrived\_B2CW; when sensor 2 (S4) is asserted, state moves to A1CCW\_B2CCW.

**Table 1**  
Table Of Outputs For Train Controller State Machine

Outputs	States							
	A1CCW - B3CCW	Aarrived - B3CCW	A1CCW - B2CCW	Aarrived - B2CCW	Aarrived - B2CW	A1CCW - B2CW	Not Used	Not Used
Sw1	X	X	1	1	0	1	X	X
Sw2	X	X	0	0	0	0	X	X
Sw3	X	X	X	X	X	X	X	X
Sw4	X	X	X	X	X	X	X	X
DA[1..0]	01	00	01	00	00	01	XX	XX
DB[1..0]	01	01	01	01	10	10	XX	XX

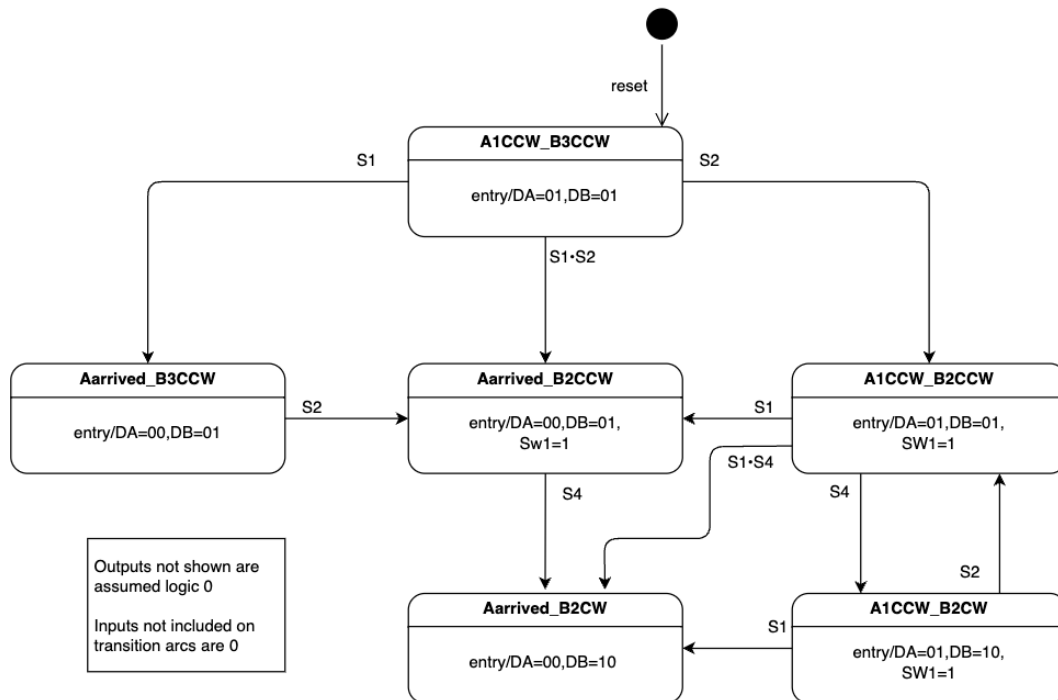

**Figure 7.** UML state diagram for Train Controller state machine meant to crash both trains at sensor 1. Initial state marked by black dot is A1CCW\_B3CCW. Crash state is Aarrived\_B2CW. Train B bounces back-and-forth on track 2 until Train A arrives at sensor 1 where it then travels clockwise on track 2 onto track 1 to crash at sensor 1.



Appendix A  
VHDL Code Implementing Train Controller Finite State Machine

```
-- State machine to control trains, adapted from class template
-- Author: Rudra Goel
-- Date 10/3/2024
```

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;
```

```
ENTITY TrainController IS
```

```
    PORT(
        reset, clock, sensor1, sensor2      : IN std_logic;
        sensor3, sensor4, sensor5, sensor6   : IN std_logic;
        switch1, switch2, switch3, switch4   : OUT std_logic;
        dirA, dirB                           : OUT
std_logic_vector(1 DOWNTO 0)
    );
END TrainController;
```

```
ARCHITECTURE a OF TrainController IS
```

```
-- Create a new TYPE called STATE_TYPE that is only allowed
-- to have the values specified here. This
-- 1) enables using helpful names for values instead of
--    arbitrary values
-- 2) ensures that signals of this type can
--    only have valid values, and
-- 3) helps the synthesis software create
--    efficient hardware for the design.
```

```
TYPE STATE_TYPE IS (
    A1CCW_B3CCW,
    A1CCW_B2CCW,
    A1CCW_B2CW,
    Aarrived_B3CCW,
    Aarrived_B2CCW,
    Aarrived_B2CW
);
```

```
-- Create a signal of the new type.
SIGNAL current_state      : STATE_TYPE;
```

```
-- This creates some new internal signals which will be
-- concatenations of some of the sensor signals.
-- This will make CASE statements easier.
```

```
SIGNAL sensor12, sensor14 : std_logic_vector(1 DOWNTO 0);
```

```

BEGIN
    -- This is the sequential logic portion that is clocked
    PROCESS (clock, reset)
    BEGIN
        IF reset = '1' THEN
            current_state <= A1CCW_B3CCW;
        ELSIF clock'EVENT and clock='1' THEN
            CASE current_state IS

                WHEN A1CCW_B3CCW =>
                    CASE sensor12 IS

                        WHEN "11" => current_state <= Aarrived_B2CCW;
                        WHEN "10" => current_state <= Aarrived_B3CCW;
                        WHEN "01" => current_state <= A1CCW_B2CCW;
                        WHEN others => current_state <= A1CCW_B3CCW;

                    END CASE;

                WHEN Aarrived_B3CCW =>
                    CASE sensor12 IS

                        WHEN "11" => current_state <= Aarrived_B2CCW;
                        WHEN others => current_state <= Aarrived_B3CCW;

                    END CASE;

                WHEN A1CCW_B2CCW =>
                    CASE sensor14 IS

                        WHEN "11" => current_state <= Aarrived_B2CW;
                        WHEN "10" => current_state <= Aarrived_B2CCW;
                        WHEN "01" => current_state <= A1CCW_B2CW;
                        WHEN others => current_state <= A1CCW_B2CCW;

                    END CASE;

                WHEN Aarrived_B2CCW =>
                    CASE sensor4 is

                        WHEN '1' => current_state <= Aarrived_B2CW;
                        WHEN others => current_state <= Aarrived_B2CCW;

                    END CASE;

                WHEN A1CCW_B2CW =>
                    CASE sensor12 is

                        WHEN "10" => current_state <= Aarrived_B2CW;

```

```

        WHEN "01" => current_state <= A1CCW_B2CCW;
        WHEN others => current_state <= A1CCW_B2CW;

        END CASE;
    WHEN Arrived_B2CW =>

        current_state <= Arrived_B2CW;

    END CASE;

END IF;
END PROCESS;

-- The following logic is NOT in a process block,
-- and thus does not depend on any clock.
-- Everything here is pure combinational
-- logic, and exists in parallel with everything else.
-- These outputs are constant values for this solution;

Switch3 <= '0';
Switch4 <= '0';

-- Combine bits for the internal signals declared above.
-- ("&" operator is concatenation)
sensor12 <= sensor1 & sensor2;
sensor14 <= sensor1 & sensor4;

--since this is moore FSM,
--the outputs only depend on the current state

WITH current_state SELECT switch1 <=
    '1' WHEN A1CCW_B2CCW,
    '1' WHEN Arrived_B2CCW,
    '0' WHEN Arrived_B2CW,
    '1' WHEN A1CCW_B2CW,
    '0' WHEN others;
WITH current_state SELECT switch2 <=
    '0' WHEN A1CCW_B2CCW,
    '0' WHEN Arrived_B2CCW,
    '0' WHEN Arrived_B2CW,
    '0' WHEN A1CCW_B2CW,
    '0' WHEN others;
WITH current_state SELECT dirA <=
    "01" WHEN A1CCW_B3CCW,
    "00" WHEN Arrived_B3CCW,

```

```

        "01" WHEN A1CCW_B2CCW,
        "00" WHEN Aarrived_B2CCW,
        "00" WHEN Aarrived_B2CW,
        "01" WHEN A1CCW_B2CW;
WITH current_state SELECT dirB <=
        "01" WHEN A1CCW_B3CCW,
        "01" WHEN Aarrived_B3CCW,
        "01" WHEN A1CCW_B2CCW,
        "01" WHEN Aarrived_B2CCW,
        "10" WHEN Aarrived_B2CW,
        "10" WHEN A1CCW_B2CW;
END a;
```