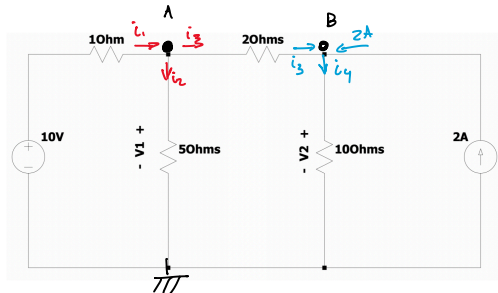


Homework 2

Friday, October 4, 2024 10:28 PM

Problem 1. Compute the voltages V_1 and V_2 in the circuit shown in Fig. 1 using the Kirchhoff's laws (KCL, KVL) and Ohm's law only.



KCL @ A
 $i_1 - i_2 - i_3 = 0$
 $\frac{10 - V_1}{10} - \frac{V_1 - 0}{50} - \frac{V_1 - V_2}{20} = 0$
 $10 - V_1 - \frac{1}{5}V_1 - \frac{1}{2}V_1 + \frac{1}{2}V_2 = 0$
 $10 + \frac{1}{2}V_2 = V_1 + \frac{1}{5}V_1 + \frac{1}{2}V_1$
 $\frac{17}{10}V_1 - \frac{1}{2}V_2 = 10$

KCL @ B
 $i_3 + 2 - i_4 = 0$
 $\frac{V_1 - V_2}{20} + 2 - \frac{V_2 - 0}{100} = 0$
 $\frac{1}{2}V_1 - \frac{1}{2}V_2 - \frac{1}{10}V_2 + 2 = 0$
 $\frac{1}{2}V_1 - \frac{6}{10}V_2 = -2$


Matrix form:

$$\begin{bmatrix} 17/10 & -1/2 \\ 1/2 & -6/10 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ -2 \end{bmatrix}$$

Solving:
 $V_1 = 100/11 = 9.09V$
 $V_2 = 120/11 = 10.91V$

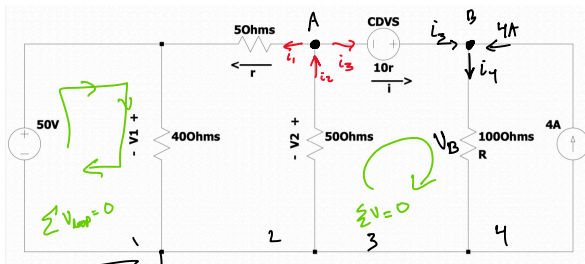Problem 2. Compute the voltages V_1 and V_2 in the circuit shown in Fig. 2 using the Kirchhoff's laws (KCL, KVL) and Ohm's law only.

Note the "CDVS" in Fig. 2 denotes *current-dependent-voltage-source*.



KVL @ A
 $i_2 - i_1 - i_3 = 0$
 $\frac{V_2 - 0}{50} - \frac{V_1 - 0}{40} - \frac{V_1 - V_2}{50} = 0$
 $\frac{V_2}{50} + \frac{V_2 - 50}{50} - \frac{V_1}{40} = 0$
 $\frac{V_2}{50} + \frac{1}{5}V_2 - 10 - \frac{V_1}{40} = 0$

KVL @ B
 $i_3 - i_4 + 4 = 0$
 $\frac{V_1 - V_2}{50} - \frac{V_2 - 0}{100} + 4 = 0$
 $\frac{V_1}{50} - \frac{3}{100}V_2 + 4 = 0$


Matrix form:

$$\begin{bmatrix} 3 & 1 & 0 \\ 1/50 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 10 \end{bmatrix}$$

Solving:
 $V_1 = 50V$
 $V_2 = 68.42V$
 $i_3 = 5.05A$

0 100 L 1 - 4

Problem 3. Compute the power associated with the 42V voltage supply in Fig. 3.

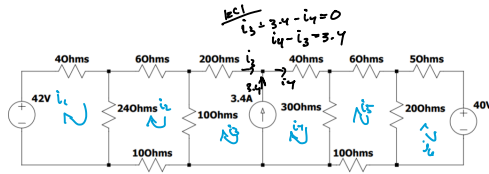

mesh 1

$$4i_1 + 24(i_1 - i_2) = 42$$

$$20i_1 - 24i_2 = 42 \quad \#$$

mesh 2

$$24(i_2 - i_1) + 6i_2 + 10(i_2 - i_3) + 10i_2 = 0$$

$$24i_2 - 24i_1 + 6i_2 + 10i_2 - 10i_3 + 10i_2 = 0$$

$$-24i_1 + 50i_2 - 10i_3 = 0 \quad \#$$

mesh 3 + 4

$$10(i_3 - i_2) + 20i_3 + 4i_4 + 30(i_4 - i_5) = 0$$

$$30i_3 - 10i_2 + 34i_4 - 30i_5 = 0$$

mesh 5

$$30(i_5 - i_4) + 6i_5 + 20(i_5 - i_6) + 10i_5 = 0$$

$$66i_5 - 30i_4 - 20i_6 = 0$$

mesh 6

$$20(i_6 - i_5) + 5i_6 = -40$$

$$25i_6 - 20i_5 = -40$$

$$\begin{bmatrix} i_1 & i_2 & i_3 & i_4 & i_5 & i_6 & b \\ 28 & -24 & 0 & 0 & 0 & 0 & 42 \\ 0 & 0 & -1 & 1 & 0 & 0 & 3.4 \\ -24 & 50 & -10 & 0 & 0 & 0 & 0 \\ 0 & -10 & 30 & 34 & -30 & 0 & 0 \\ 0 & 0 & 0 & -30 & 66 & -20 & 0 \\ 0 & 0 & 0 & 0 & -20 & 25 & -40 \end{bmatrix}$$

Solved in matrix





$$i_1 = 2.12 \text{ A}$$


P_{42V}

$$P_{42V} = 2.12 \cdot 42 = 89.04 \text{ W}$$


Problem 4. With clear derivations and corresponds circuits, find the Norton equivalent circuit with respect to the terminals a, b for the circuit shown in Fig. 4.

R_N ✓
 I_N ✓

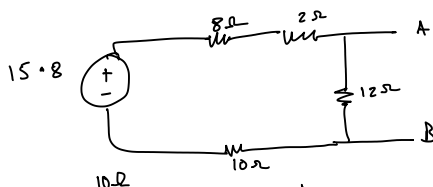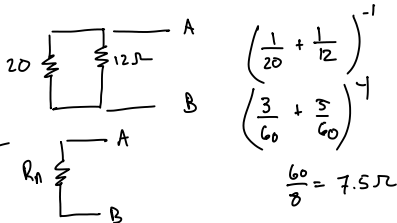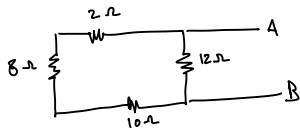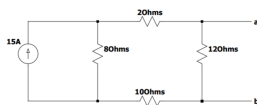

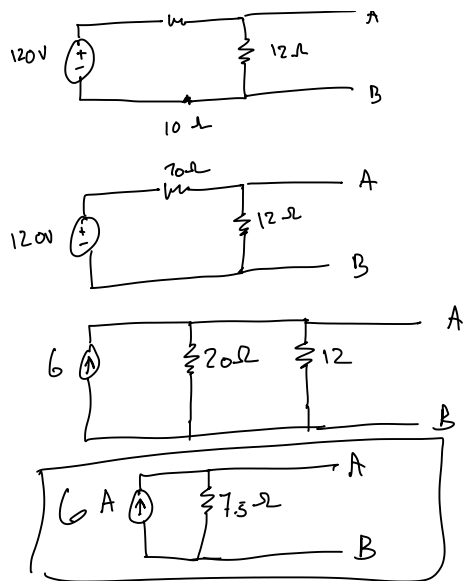














Problem 5. A Voltmeter with an internal resistance (IR) of 100K Ohms is used to measure the voltage V_0 in the circuit shown in Fig. 5 below. With clear derivations and corresponds circuits, find the Voltmeter reading for V_0 using the source transform method.

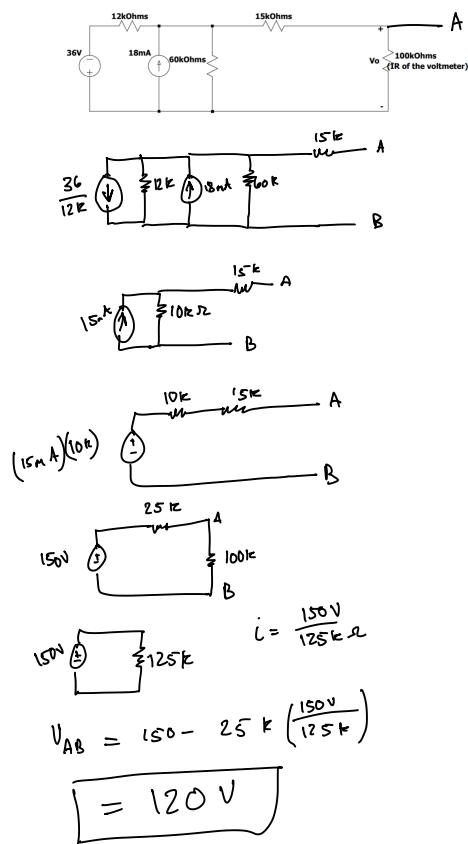


Problem 6. With clear derivations and corresponds circuits, find the Thevenin and Norton equivalent circuits with respect to the terminals a, b for circuit shown in Fig. 6.


$$R_N = 27.1797 \Omega$$

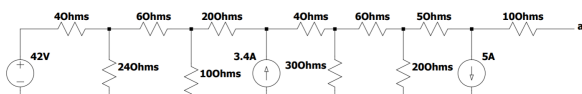

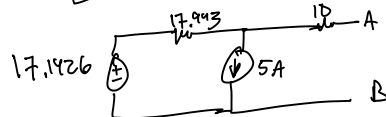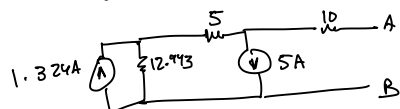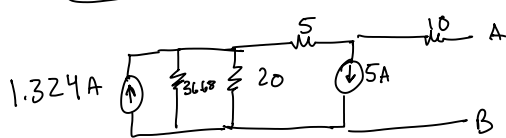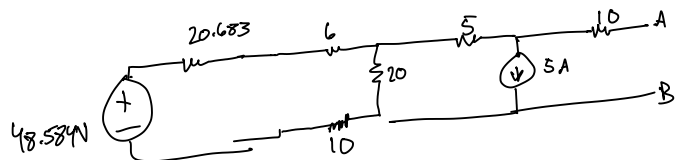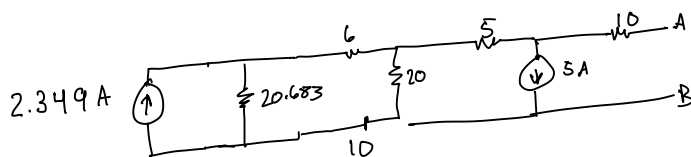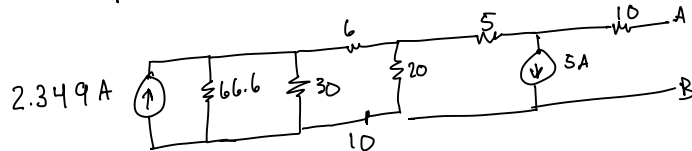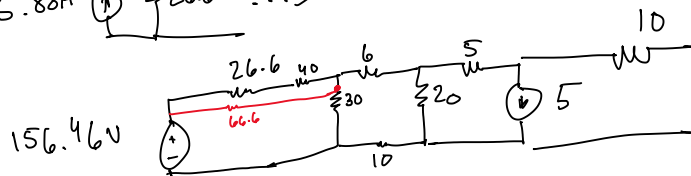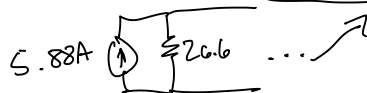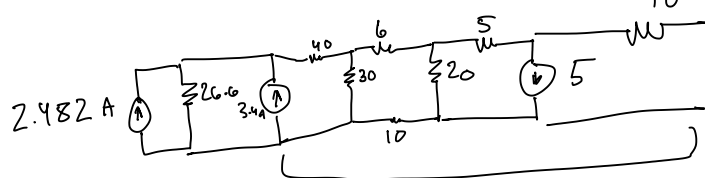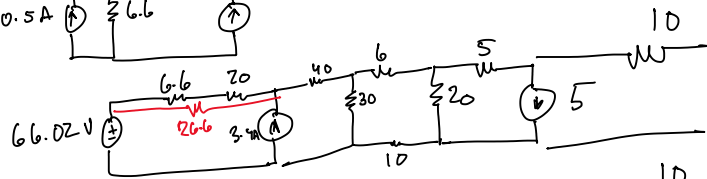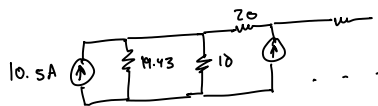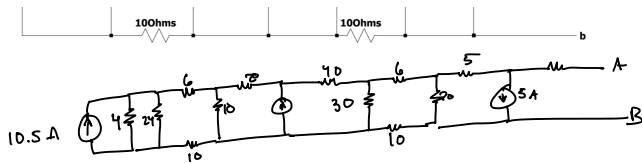


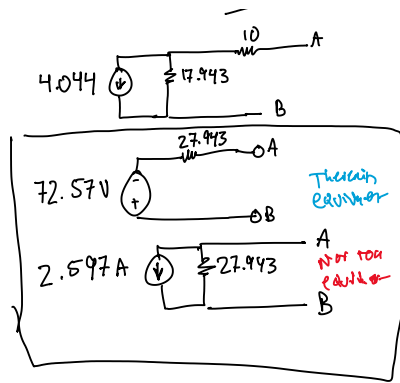

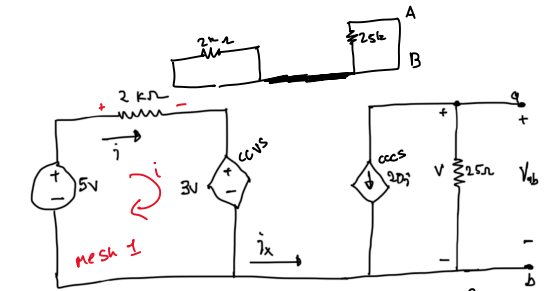Problem 7. Derive the Thevenin and Norton equivalent circuits from the circuit shown below.



$$-5V + 2000i + 3V_{ab} = 0$$

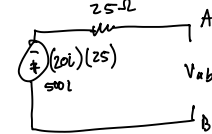

$$V_{ab} = 500i$$

$$i = \frac{V_{ab}}{500}$$

$$-5V + 2000 \left[\frac{V_{ab}}{500} \right] + 3V_{ab} = 0$$

$$7V_{ab} = 5$$

$$V_{ab} = \frac{5}{7}V$$

$$i = \frac{5}{7} \cdot \frac{1}{500} = \frac{1}{700} = .0014285A$$

