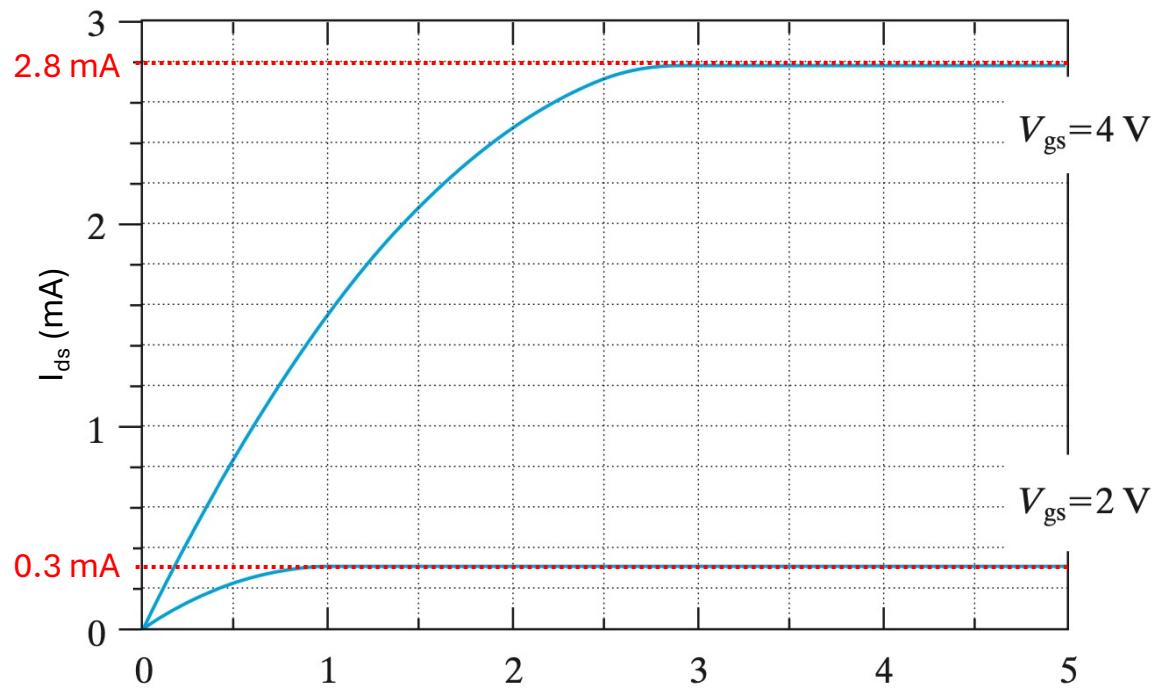


1. (20 points) The output characteristics of a MOSFET are shown below.

- (8 points) From the I-V characteristics below, determine the threshold voltage of the device by comparing the saturation current for the two operating conditions.
- (7 points) Find the Beta-factor (β) of the device.
- (5 points) Determine the drain current of the device when $V_{ds} = 2V$ and $V_{gs} = 3.5V$.



c) I_{DS} for Saturation is

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_{th})^2$$

$$\frac{I_{DS1}}{I_{DS2}} = \frac{\frac{\beta}{2} (V_{GS1} - V_t)^2}{\frac{\beta}{2} (V_{GS2} - V_t)^2} \Rightarrow \frac{2.8\text{ mA}}{0.3\text{ mA}} = \frac{(4 - V_t)^2}{(2 - V_t)^2}$$

$$\sqrt{9.33} = \frac{4 - V_t}{2 - V_t} \Rightarrow 3.055 = \frac{4 - V_t}{2 - V_t}$$

$$6.11 - 3.055V_t = 4 - V_t$$

$$2.055V_t = 2.11$$

$$V_t = 1.0267V^2$$

$$b) I_{DS} = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

$$I_{DS} = .0028 = \frac{\beta}{2} (4 - 1.0267)^2$$

$$\boxed{\beta = 0006334849 \text{ A/V}^2}$$

$$c) V_{DS} = 2 \text{ V} \quad V_{GS} = 3.5 \text{ V}$$

$$3.5 - V_{TH} = 2.47$$


$V_{DS} < V_{GS} - V_{TH}$
=> Linear Region

$$I_{DS} = \beta \left[(V_{GS} - V_T) - \frac{V_{DS}}{2} \right] V_{DS}$$
$$\beta \left(2.47 - \frac{1}{2} \right) (2)$$

$$\boxed{= .0025 \text{ A} = I_{DS}}$$

Symmetric

2. (a) (10 points) Consider the inverter circuit shown below. Assume that $V_{tn} = |V_{tp}|$.
- (2 points) Draw the VTC of the inverter.
 - (2 points) Write down the relationship between V_{in} and V_o using voltage division.
 - (3 points) On the same graphs as (i) now sketch the relationship between V_{in} and V_o through the resistor network.
 - (3 points) From these two plots show the final voltage where the output, V_o settles down (equilibrium point). Assume that the value of R_2 is very high and it does not disrupt the normal operation of the inverter.

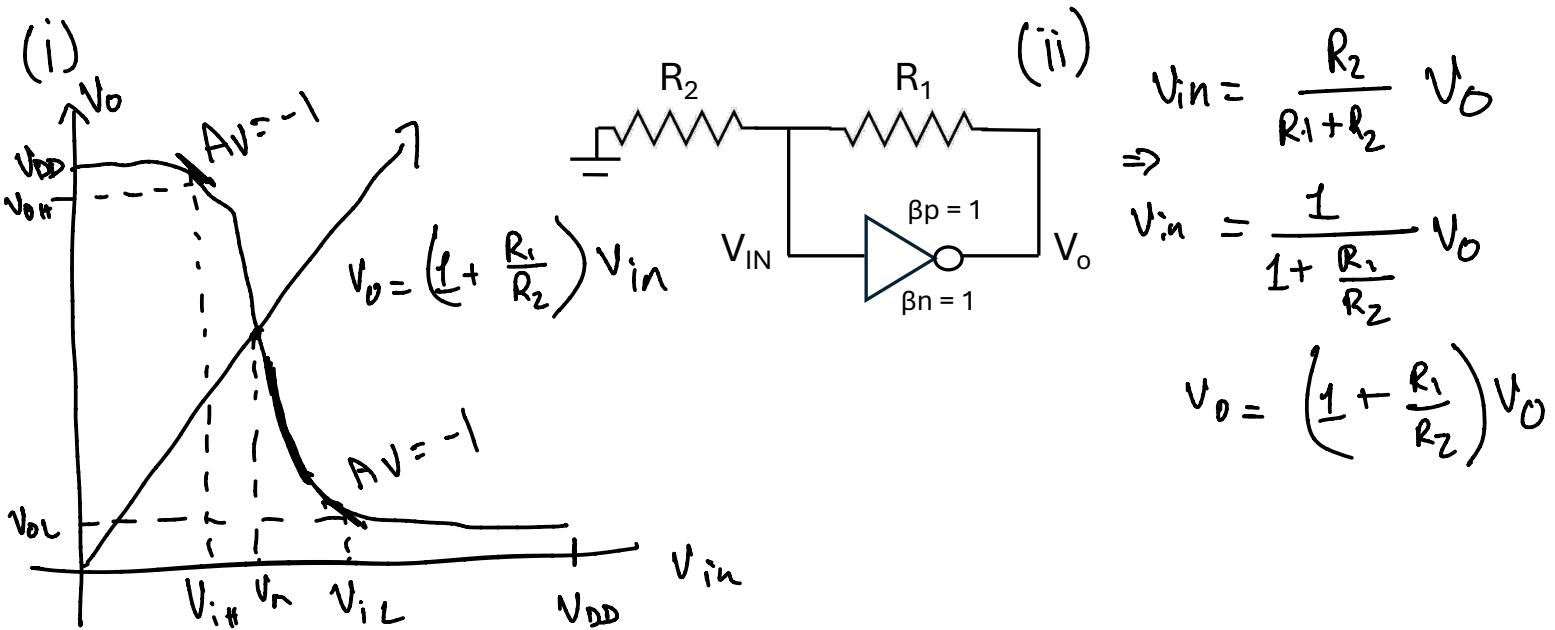

(IV) if $R_2 \gg R_1 \Rightarrow V_o = (1) V_{in}$

$$V_M = \frac{V_{DD} - |V_{tp}| + |V_{tn}|}{2}$$

$$\text{since } \sqrt{\frac{B_n}{B_p}} = 1$$

$$V_M = \frac{1}{2} V_{DD}$$

\Rightarrow equilibrium point is intersection of V_o w.r.t. V_{in} and VTC of inverter

$$\Rightarrow \boxed{V_o = \frac{1}{2} V_{DD}}$$

(b) (10 points) In part (a), if R_1 is a variable resistor and its value increases, how does the final value of V_o change? What is V_o for the two limiting cases: (i) when R_1 is 0, and (ii) when R_1 is ∞

Given that $V_o = \left(1 + \frac{R_1}{R_2}\right) V_{in}$ By Voltage Division

V_o will increase as R_1 increases.

(i) When R_1 is 0, $V_o = V_{in}$

and the intersection of the curves in 2a(III) will be $\frac{1}{2}$ the supply voltages (V_m or tripping point of inverter)

(ii) When $R_1 \rightarrow \infty$ $\lim_{R_1 \rightarrow \infty} V_o = \infty$, But in our case, the slope will grow to ∞ or practically a vertical line. This means that V_o will be the supply voltage fully when R_1 is ∞ and will behave like a standard inverter.

3. (a) (12 points) Consider an NMOS transistor with $\beta_n = 0.2 \text{ mA/V}^2$ and $V_{tn} = 0.5\text{V}$ and the following terminal voltages. Identify the region of operation of the device in each of these configurations and determine the current through the device in these configurations:

- i. $V_G = 1.2 \text{ V}$, $V_D = 0.8 \text{ V}$, $V_S = 0.2 \text{ V}$
- ii. $V_G = 0.5 \text{ V}$, $V_D = 0.9 \text{ V}$, $V_S = 0.1 \text{ V}$
- iii. $V_G = 1.0 \text{ V}$, $V_D = 0.4 \text{ V}$, $V_S = 0.2 \text{ V}$

$$(i) \quad V_g = 1.2 \text{ V} \quad V_D = 0.8 \text{ V} \quad V_S = 0.2 \text{ V}$$

$$V_{GS} = 1 \text{ V} \quad V_{DS} = 0.6 \text{ V} \quad V_{gt} = V_{GS} - V_{tn} = \frac{1}{2}$$

$V_{GS} > V_{tn} \rightarrow \text{Device ON}$

$V_{DS} > V_{GS} - V_{tn} \rightarrow \text{Saturation Region}$

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_{tn})^2 \Rightarrow \frac{0.2}{2} \left(\frac{1}{2}\right)^2 = 0.025 \text{ mA}$$

$$(ii) \quad V_g = 0.5 \quad V_D = 0.9 \quad V_S = 0.1 \quad I_{DS} = 0.025 \text{ mA}$$

$$V_{GS} = 0.4 \text{ V} \quad V_{DS} = 0.8 \text{ V}$$

$V_{GS} < V_{tn} \rightarrow \text{Device off} \Rightarrow \text{Cut-off Region}$

$$I_{DS} \approx 0 \text{ A}$$

$$(iii) \quad V_g = 1 \quad V_D = 0.4 \quad V_S = 0.2 \quad V_{gt} = V_{GS} - V_{tn} = 0.7 - 0.5 = 0.2$$

$$V_{GS} = 0.8 \quad V_{DS} = -0.2$$

$V_{GS} > V_{tn} \rightarrow \text{On}$

$V_{DS} < V_{gt} \Rightarrow \text{Linear Region}$

$$I_{DS} = 0.5 \left[(0.8 - 0.5) - 0.1 \right] (0.2) = 0.025 \text{ mA}$$

$$V_M = \frac{V_{DD} - |V_{tP}| + \sqrt{\beta_n/\beta_p} V_{tn}}{1 + \sqrt{\beta_n/\beta_p}}$$

(b) (8 points) A CMOS inverter is designed with NMOS and PMOS transistors where $V_{tn} = |V_{tP}| = 0.6V$. Assume $V_{DD} = 3.3V$.

What is the inverter switching threshold (also called the trip point, V_M) voltage for the following three cases:

- $\beta_n = 0.250 \text{ mA/V}^2$, $\beta_p = 0.125 \text{ mA/V}^2$ 2
- $\beta_n = 0.125 \text{ mA/V}^2$, $\beta_p = 0.250 \text{ mA/V}^2$ Y2
- $\beta_n = 0.250 \text{ mA/V}^2$, $\beta_p = 0.250 \text{ mA/V}^2$ 1

Comment on how the inverter's V_M changes as the β -factor changes.

$$\text{Case 1: } \sqrt{\beta_n/\beta_p} = \sqrt{0.250/0.125} = \sqrt{2}$$

$$V_M = \frac{3.3 - 0.6 + \sqrt{2}(0.6)}{1 + \sqrt{2}} = \boxed{1.4698 \text{ V}}$$

$$\text{Case 2: } \sqrt{\beta_n/\beta_p} = \sqrt{0.125/0.250} = \frac{\sqrt{2}}{2}$$

$$V_M = \frac{3.3 - 0.6 + \frac{\sqrt{2}}{2}(0.6)}{1 + \frac{\sqrt{2}}{2}} = \boxed{1.8301 \text{ V}}$$

$$\text{Case 3: } \sqrt{\beta_n/\beta_p} = 1$$

$$V_M = \frac{3.3 - 0.6 - 0.6}{2} = \boxed{1.65 \text{ V}}$$

- When the ratio of β_n/β_p is greater than 1, the tripping point is less than $V_{DD}/2$.
- Whereas when the Ratio is less than 1, the tripping point is greater than $V_{DD}/2$.
When β_n/β_p is not 1, there is bias in the inverter characteristics.

4. (20 points) The output conductance of an NMOS represents the sensitivity of the drain current, I_{ds} to the drain-to-source voltage, V_{ds} . It is given by the following:

$$g_{ds} = \frac{\partial I_{ds}}{\partial V_{ds}}$$

- a) Consider that the NMOS is operating in the linear region. Derive an expression for the output conductance.
- b) If the Beta-factor is given as $\beta = 0.2 \text{mA/V}^2$, determine the output conductance when $V_{gs} = 3.3 \text{V}$, $V_T = 1.2 \text{V}$ and $V_{ds} = 1.0 \text{V}$.
- c) As the V_{ds} increases, the NMOS approaches saturation. How does the output conductance change?
- d) Derive an expression for (g_m/g_{ds}) of the transistor in the linear region in the condition when $V_{ds} \ll (V_{gs} - V_T)$. Here:

a) $g_{ds} = \frac{\partial I_{DS}}{\partial V_{DS}}$

$$g_m = \frac{\partial I_{ds}}{\partial V_{gs}}$$

$$I_{DS} = \beta \left[V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS}$$

$$\boxed{g_{ds} = \beta (V_{GS} - V_{TN}) - \frac{1}{2} \beta V_{DS}}$$

b) $g_{ds} = 0.2 (3.3 - 1.2 - 0.25) \Rightarrow \boxed{0.37 \frac{\text{mA}}{\text{V}}}$

c) As V_{DS} grows, g_{ds} decreases and eventually reaches zero as $\frac{\partial I_{DS}}{\partial V_{DS}}$ is zero for a NMOS operating in saturation as

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_{TN})^2, \text{ no } V_{DS} \text{ to different on.}$$

$$D) I_{DS} = \beta \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$

When $V_{DS} \ll V_{GS} - V_{th}$ can be omitted

$$I_{DS} = \beta (V_{GS} - V_{th}) V_{DS}$$

$$g_{DS} = \frac{\partial I_{DS}}{\partial V_{DS}} = \beta (V_{GS} - V_{th})$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \beta V_{DS}$$

$$\frac{g_m}{g_{DS}} = \frac{\beta V_{DS}}{\beta (V_{GS} - V_{th})} \Rightarrow \boxed{\frac{V_{DS}}{V_{GS} - V_{th}}}$$

5. (20 points) In the circuit of a non-ideal resistive inverter shown below the NMOS transistor has the following parameters:

$$\beta_n = 2m A/V^2; V_T = 1V.$$

- (i) (12 points) Determine the voltage V_O when the transistor operates in saturation
 (ii) (8 points) Determine the maximum value of R_D needed to ensure that transistor operates in saturation.

(i) When in Saturation
 The Device is
 On $\Rightarrow I_1 = I_2$

$$V_O = \frac{R_S}{R_D + R_S} (V_{in} - V_{th})$$

$$= \frac{1}{1 + \frac{R_D}{R_S}} \quad 4$$

$$V_O = \frac{1}{1 + \frac{R_D}{1000}}$$

$$I_{DS} = (2)(2 - I_{DS}(1000))^2$$

$$I_{DS} = 2 - 4000 I_{DS} + 1000^2 I_{DS}$$

$$V_O = I_{DS}(1000) \boxed{8V}$$

