

Homework 3

Thursday, October 17, 2024 4:24 PM

2

Problem 1. Assume that the op amp in the circuit shown in Fig. 1 is ideal.

- 1) Calculate V_o for the following values of V_s : 0.4, 2.0, 3.5, -0.6, -1.6, and -2.4 V.
- 2) Specify the range of V_s required to avoid amplifier saturation.

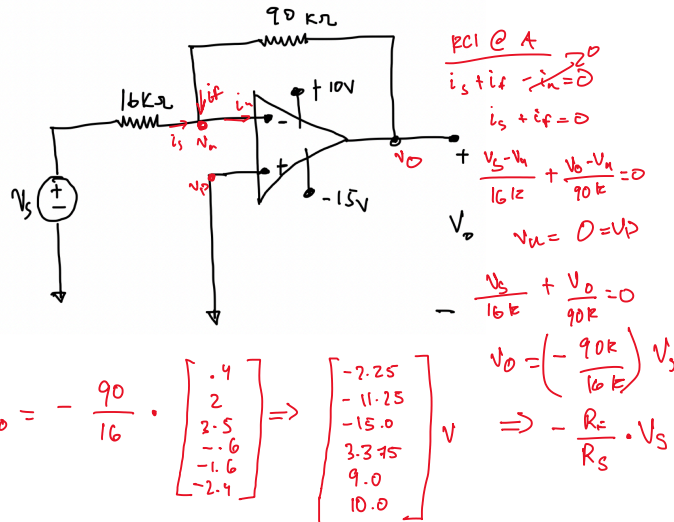


Fig. 1.

$$1) V_o = - \frac{90}{16} \cdot \begin{bmatrix} .4 \\ 2 \\ 2.5 \\ -.6 \\ -1.6 \\ -2.4 \end{bmatrix} \Rightarrow \begin{bmatrix} -2.25 \\ -11.25 \\ -15.0 \\ 3.375 \\ 9.0 \\ 10.0 \end{bmatrix} V \Rightarrow - \frac{R_f}{R_s} \cdot V_s$$

- 2) Since the max an ideal op amp can amplify is determined by the supply voltages

The bounds of V_s are

$$-15 \leq V_o \leq 10$$

$$-15 \leq 5.625 V_s \leq 10$$

$$2.67 \geq V_s \geq -1.77 V$$

3

Problem 2. With a source voltage of -640 mV, what range of R_x allows the inverting amplifier (see Fig. 2) to operate in its linear region?

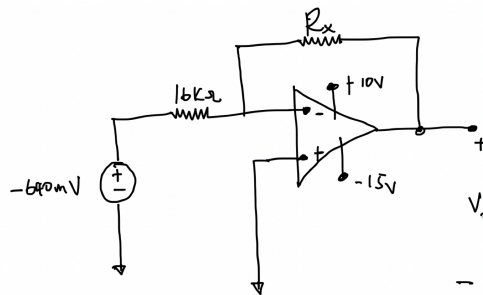


Fig. 2.

V_o is bounded by 10 and -15 as that is what the V_{cc} and V_{ee} supplies are.

$$V_o \leq 10$$

$$V_o = - \left[\frac{R_f}{R_s} \right] \cdot V_s$$

$$\left(\frac{R_x}{16k} \right) (.64) \leq 10$$

$$V_o = - \left[\frac{R_x}{16k} \right] (-.640)$$

$$= R_x \left(\frac{.64}{16k} \right)$$

$$10 \leq R_x \leq 250k\Omega$$


$$-15 \leq V_o \leq 10$$

$$- \frac{R_f}{R_s} V_s$$

$$+ \frac{R_x}{16k} (640mV) \leq 10$$

Problem 3.

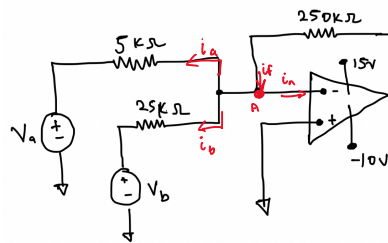- 1) Find V_o in the circuit shown below if $V_a = 0.1$ V and $V_b = 0.25$ V.
- 2) If $V_b = 0.25$ V, how large can V_a be before the op amp saturates?
- 3) If $V_a = 0.10$ V, how large can V_b be before the op amp saturates?
- 4) Repeat (a), (b), and (c) with the polarity of V_b reversed.



KCL @ A

$$i_a + i_b + i_{in} = 0 \quad i_{in} = 0$$

$$\frac{V_a - V_+}{5k} + \frac{V_a - V_+}{25k} - \frac{V_o - V_+}{250k} = 0$$

$$V_+ = 0 = V_p$$

$$\frac{-V_a}{5k} - \frac{V_a}{25k} - \frac{V_o}{250k} = 0$$

$$V_o = \left(\frac{V_a}{5k} + \frac{V_a}{25k} \right) (-250k)$$

$$V_o = \left(\frac{.1}{5k} + \frac{.25}{25k} \right) (-250k)$$

$$= -7.5 \text{ V}$$

Fig. 3.

$$\textcircled{2} V_o = \left(\frac{V_a}{5k} + \frac{.25}{25k} \right) (-250k)$$

$$\frac{-10}{-250k} = \left(\frac{V_a}{5k} + \frac{.25}{25k} \right) \Rightarrow V_a = \left(\frac{10}{250k} - \frac{.25}{25k} \right) 5k$$

$$V_a = .15 \text{ V MAX}$$

$$\textcircled{3} V_o = \left(\frac{.1}{5k} + \frac{V_b}{25k} \right) (-250k)$$

$$\frac{-10}{-250k} = \left(\frac{.1}{5k} + \frac{V_b}{25k} \right) \Rightarrow V_b = \left(\frac{10}{250k} - \frac{.1}{5k} \right) (25k)$$

$$V_b = .5 \text{ V MAX}$$

④ Reversing the polarity of V_b results in the original eqn

$$\text{TO BE } \textcircled{1} V_o = \left(\frac{V_a}{5k} - \frac{V_b}{25k} \right) (-250k) \Rightarrow \left(\frac{.1}{5k} - \frac{.25}{25k} \right) (-250k) = -2.5 \text{ V}$$


$$\textcircled{2} V_o = \left(\frac{10}{250k} + \frac{.25}{25k} \right) (5k) = 1.25 \text{ V}$$

$$\textcircled{3} V_b = \left(\frac{10}{250k} - \frac{.1}{5k} \right) (-25k) = -2 \text{ V MAX}$$

$$\left(\frac{15}{-250k} - \frac{.1}{5k} \right) (+25k) = V_b$$

Problem 4. A realistic (non-ideal) non-inverting operational amplifier model has been provided in the Fig. 4.

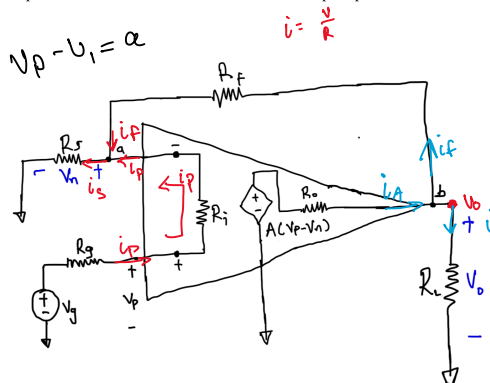- (a) Express the output voltage V_o as a function of the source voltage V_s .
- (b) Define conditions upon which the relationship between the output voltage and source voltage in this realistic op amp model will be similar to that of the ideal op amp model studied in class.



$$\left[(R_f + R_s) + \left(R_s R_o / A R_i \right) \right]$$

$$R_s + \frac{R_o}{A} \left(1 - \frac{R_f}{R_i} \right)$$

Fig. 4. A non-inverting amplifier circuit

Hint: Note that the input-output voltage relationship for an ideal non-inverting amplifier (as studied in class) can be expressed as:

$$V_o = \frac{R_s + R_f}{R_s} V_g \quad (1)$$

KCL @ A

$$i_p + i_f - i_s = 0$$

$$\frac{V_g - V_n}{R_g + R_i} + \frac{V_o - V_n}{R_f} - \frac{V_n}{R_s} = 0$$

$$\left(\frac{1}{R_g + R_i}\right) V_g + \left(-\frac{1}{R_g + R_i} - \frac{1}{R_s} - \frac{1}{R_f}\right) V_n + \frac{1}{R_f} V_o = 0$$

$$\frac{V_g}{R_g + R_i} + \frac{V_o}{R_f} = \left(\frac{1}{R_g + R_i} + \frac{1}{R_s} + \frac{1}{R_f}\right) V_n \quad (i)$$

KCL @ B

$$i_a - i_f - i_o = 0$$

$$\frac{A(V_o - V_n) - V_o}{R_o} - \left(\frac{V_o - V_n}{R_f}\right) - \frac{V_o}{R_L} = 0$$

$$\frac{A(V_o - V_n)}{R_o} + \frac{V_n}{R_f} = \frac{V_o}{R_o} + \frac{V_o}{R_L} + \frac{V_o}{R_f} \quad (ii)$$

$$V_p - V_g = (V_n - V_g) \left(\frac{R_f}{R_g + R_i}\right) \quad (iii) \rightarrow \text{FROM VOLTAGE DIVIDER}$$

$$V_p = \frac{(V_n - V_g) R_f}{R_g + R_i} + V_g \Rightarrow \left(\frac{R_i + R_s}{R_i + R_s + R_g}\right) V_g$$

$$V_n = \left(\frac{R_s}{R_g + R_s + R_i}\right) V_g$$

$$V_o \left(\frac{1}{R_o} + \frac{1}{R_L} + \frac{1}{R_f}\right) = \frac{A(V_o - V_n) R_f}{R_o R_f} + \frac{V_n R_o}{R_o R_f}$$

$$V_o = \left[\frac{A \left(\frac{(R_i + R_s) V_g}{R_i + R_s + R_g} - \frac{R_s V_g}{R_g + R_s + R_i} \right) R_f + \frac{V_g R_s R_o}{R_g + R_s + R_i}}{R_o R_f} \right]$$

$$\frac{1}{R_o} + \frac{1}{R_L} + \frac{1}{R_f}$$

- b) The positive and negative terminals will have no current flowing through them and their voltages will be equal. In other words, R_i must be $> 2 \text{ M}\Omega$ and R_o must be very small for this OP amp to be considered ideal.

$$A \rightarrow \infty$$

KCL @ node a

$$\frac{V_a - 0}{R_s} + \frac{V_a - V_b}{R_f} + \frac{V_a}{R_i}$$

KCL @ B

$$\frac{V_b - 0}{R_L} + \frac{V_b - A(V_i)}{R_o} +$$

$$V_a = V_p - V_i \Rightarrow V_p = V_g + \frac{R_f R_i}{R_i + R_f} V_i$$

$$V_i = V_n \Rightarrow \frac{V_a - V_i}{R_i + R_f}$$

same node

$$V_i = V_g + R_f + \frac{V_a - V_g}{R_i + R_f} - V_a$$

