

Appendix B: Answer Sheet

1: 14.82 V

2: -14.82 V

3: 973Ω

4: 5%

5: Yes. Resistance should be within $\pm 50 \Omega$

6: 1961Ω

7: 5 V

8: 4.92 V

9: $\left(\frac{0.08}{5}\right)(100) = 1.6 \%$

10: Resistance of wires + defect of resistor.

11: $492/973 = 5.06 \text{ mA}$

12: 4.99 mA

13: $\left(\frac{0.0763}{5.0623}\right) \cdot 100 = 1.38 \%$

14: Ammeter in series since the deviation measured from this method is smaller than using voltage probe in parallel. Additionally current in series is constant.

15: We would use the DMM to find the voltage across the resistor. Knowing this resistance and voltage, use Ohm's Law $\frac{V}{R} = i$ to obtain the current passing through the resistor.